

WELCOME

TO Adda247

# APP FEATURES



**Download Now**  
**Adda247 APP**



**Premium Study Material**



**Current Affairs**



**Job Alerts**



**Daily Quizzes**



**Subject-wise Quizzes**



**Magazines**



**Power Capsule**



**Notes & Articles**



**Videos**



# KVS TGT WVE



# MAHA MARATHON



PRE EXAM

**BEFORE REAL EXAM**

EE & EC



Q

A dynamometer type wattmeter can be used on

- (a) dc only
- (b) ac only
- (c) rectified ac only
- (d) ac as well as dc

Measurement of power

AC + dc

$$P_{avg} = VI \cos \phi$$



Q


Which of the following instruments is an integrating type instrument?

(a) Wattmeter

(b) Energy Meter

(c) Power Factor Meter


(d) None of the above

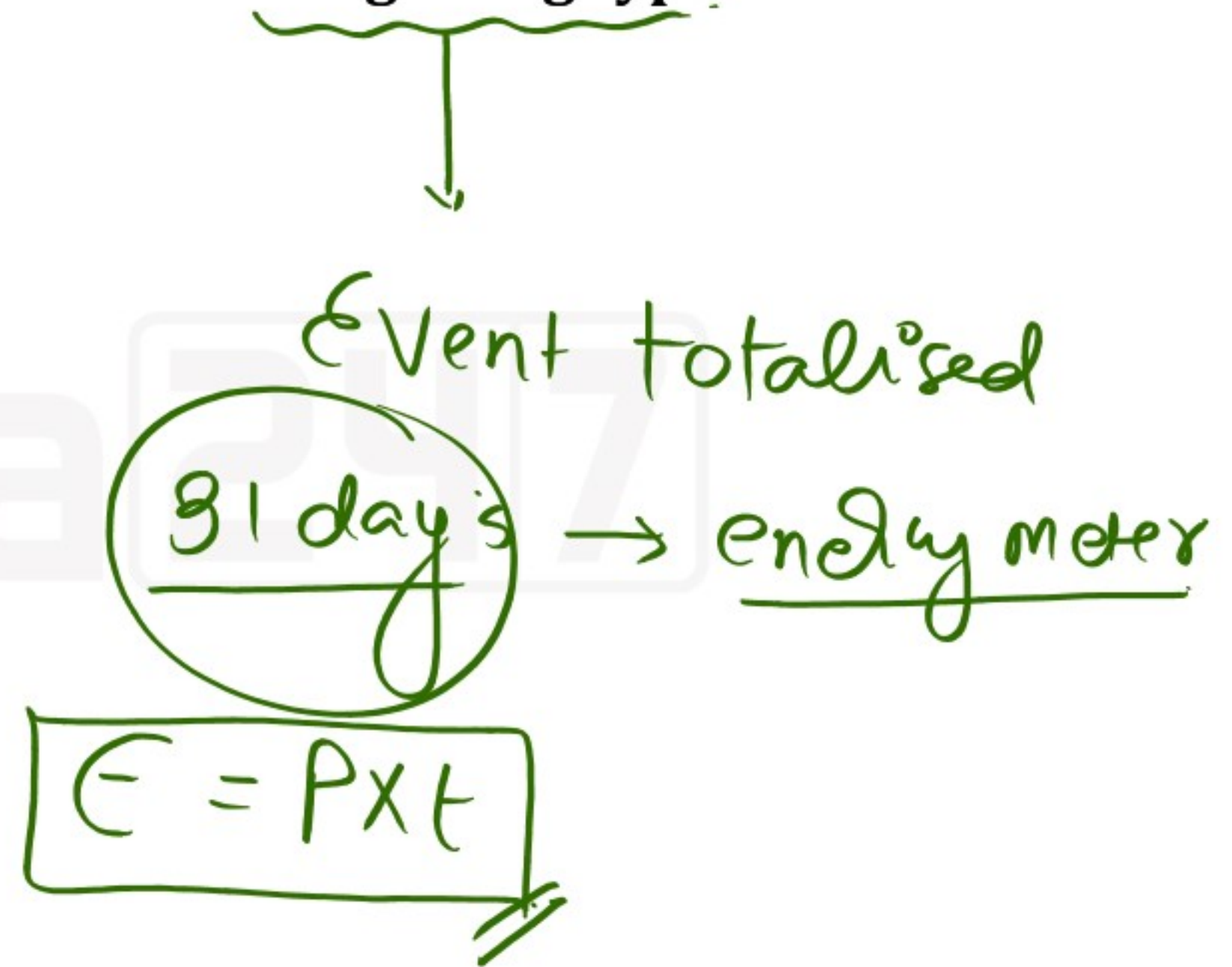

Q

The scale of power factor meter instrument is

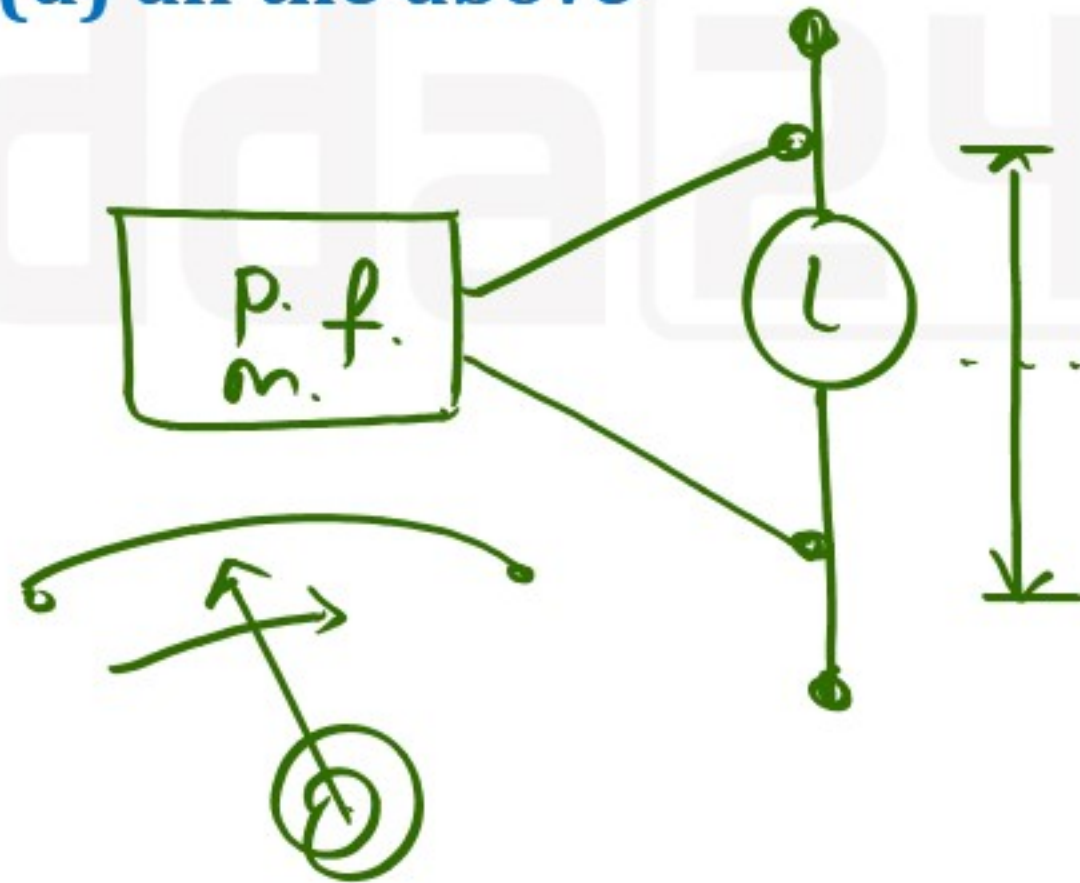- (a) Non Uniform
- (b) exponential
- (c) linear
- (d) all the above



$$P.f = \cos \phi$$

$\theta \propto \text{P.f. Angle}$   
 $\theta = \text{deflection of pointer}$



Q

①

★

A dc ammeter has resistance of  $0.1 \Omega$  and current range is  $0 - 100 \text{ A}$ . If the range is to be extended to  $0 - 500 \text{ A}$ , then meter requires shunt resistance of

- (a)  $0.010 \Omega$   
 (b)  $0.011 \Omega$   
 (c)  $0.025 \Omega$   
 (d)  $1.0 \Omega$


 $R_{sh}$ 

margin's

$$\alpha = 100$$

$$\alpha = 0.0004 \text{ :c}$$

$$R_{sh} = \frac{0.1}{5-1}$$

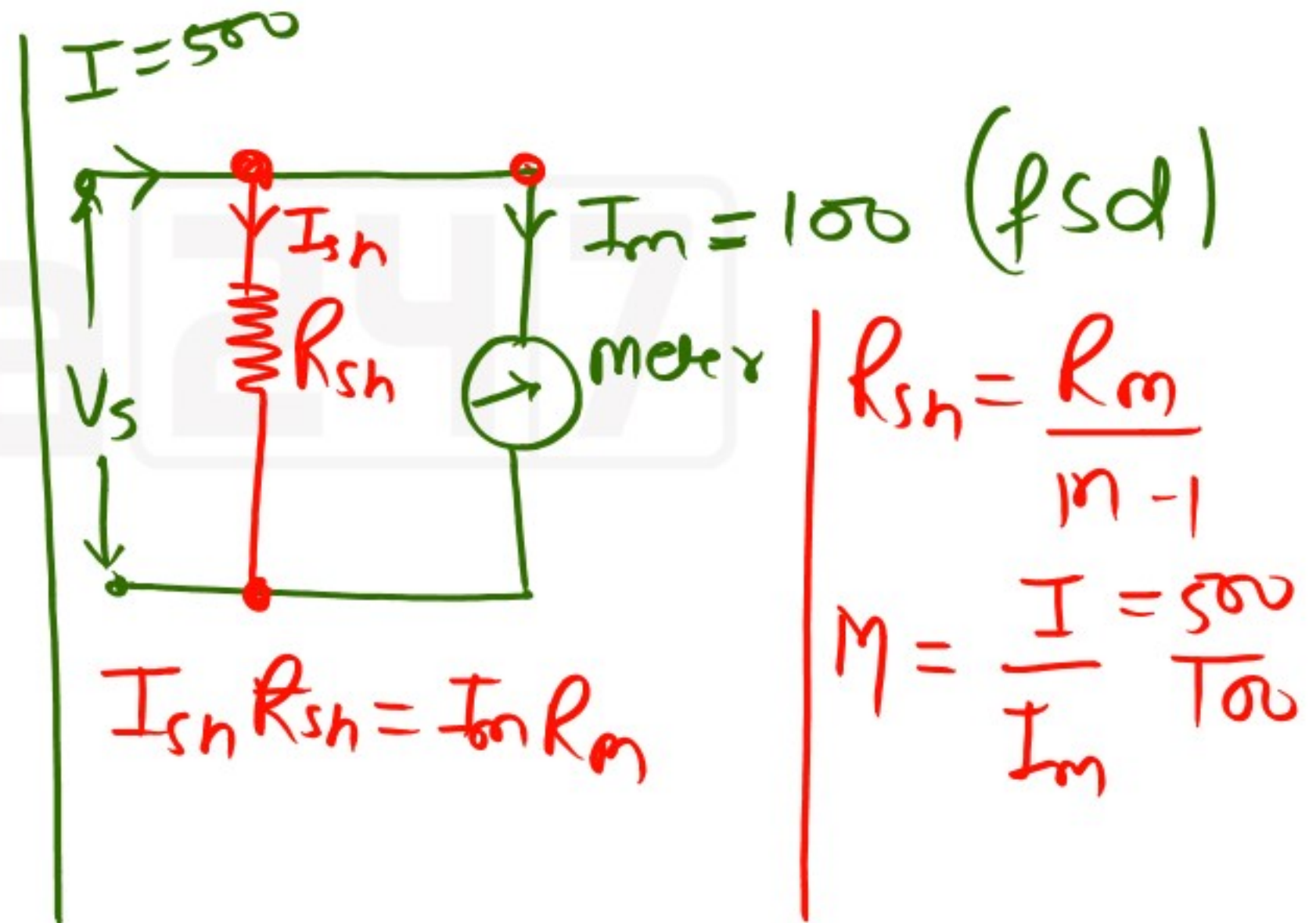

$$R_{sh} = \frac{R_m}{n-1}$$

$$n = \frac{I = 500}{I_m = 100}$$

Q

Megger is an instrument to measure

- (a) a very low resistance
- (b) insulation resistance
- (c) Q of coil
- (d) inductance of coil

Cable,  
Motor,  
Transformer





Q

Which instrument has the lowest resistance?

(a) Ammeter

(b) Voltmeter

(c) Megger

(d) Frequency - meter

→ series  
→ parallel

$$P_a = I_a^2 R_a$$

$$R_a = 0 \text{ (ideal)}$$

$$R_a = \text{low}$$

$$P_v = \frac{V^2}{R_v}$$

$$R_v = \infty \text{ (ideal)}$$

$$R_v = \text{High}$$

Q

**The moving coil in a dynamometer wattmeter is connected**

- (a) in series with the fixed coil.**
- (b) across the supply.**
- (c) in series with the load.**
- (d) any one of the above.**




P.C

↳ highly Res.

↳  $I_p$  - nearly in phase

voltage

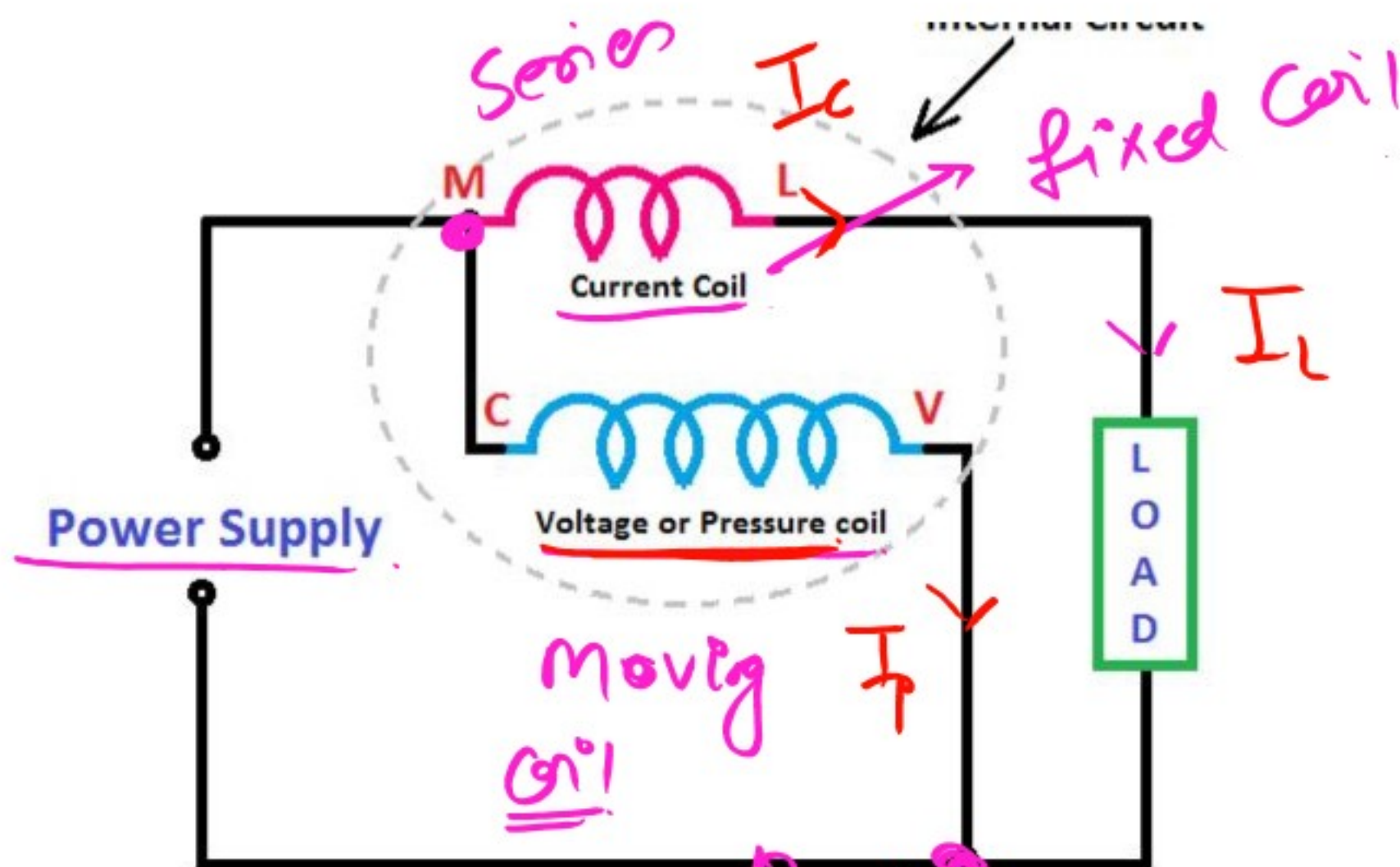

\*  $I_c \rightarrow$  lead, lag, vpf

parallel with supply.

Q

Temp. error



To increase the range of a voltmeter

(a) a low resistance is connected series.

(b) a low resistance is connected in parallel.


(c) a high resistance is connected in series.

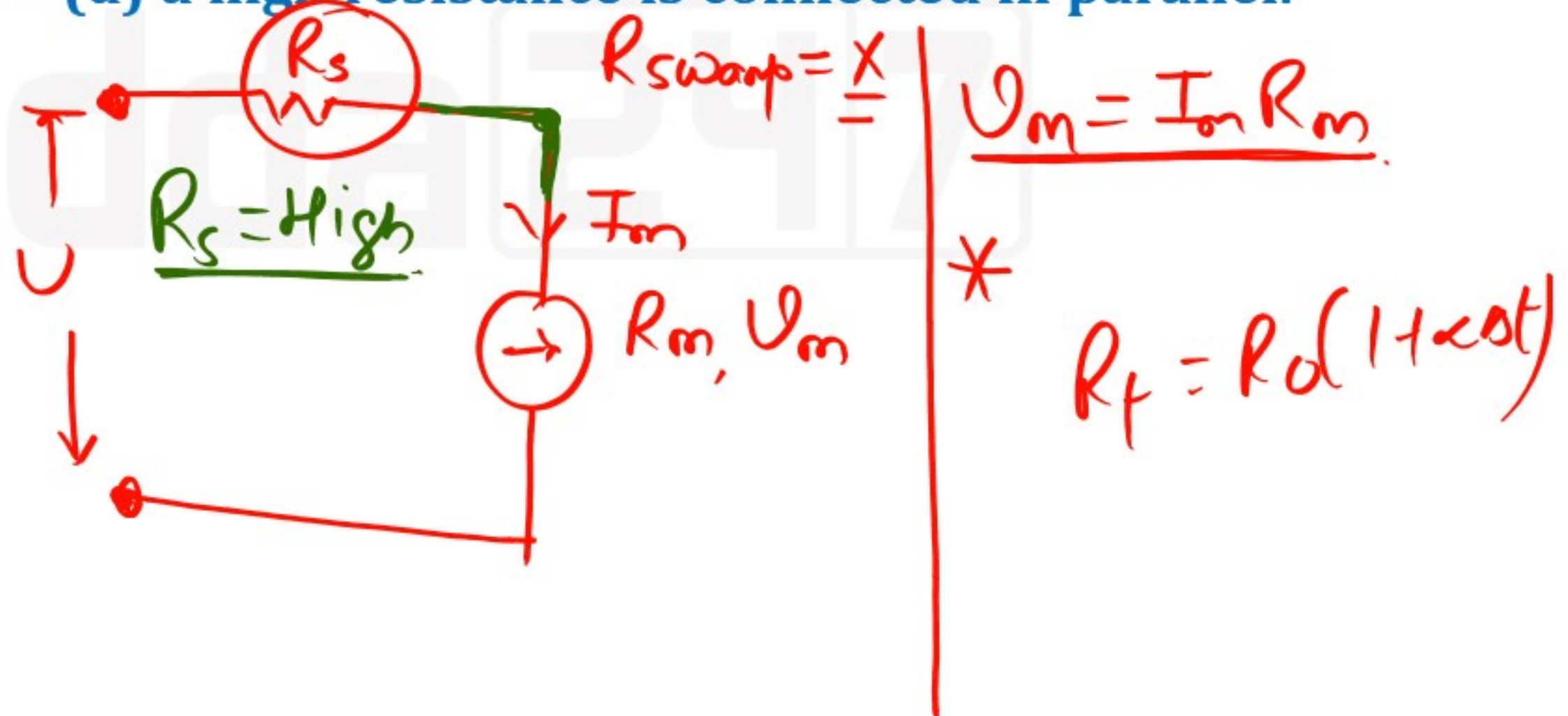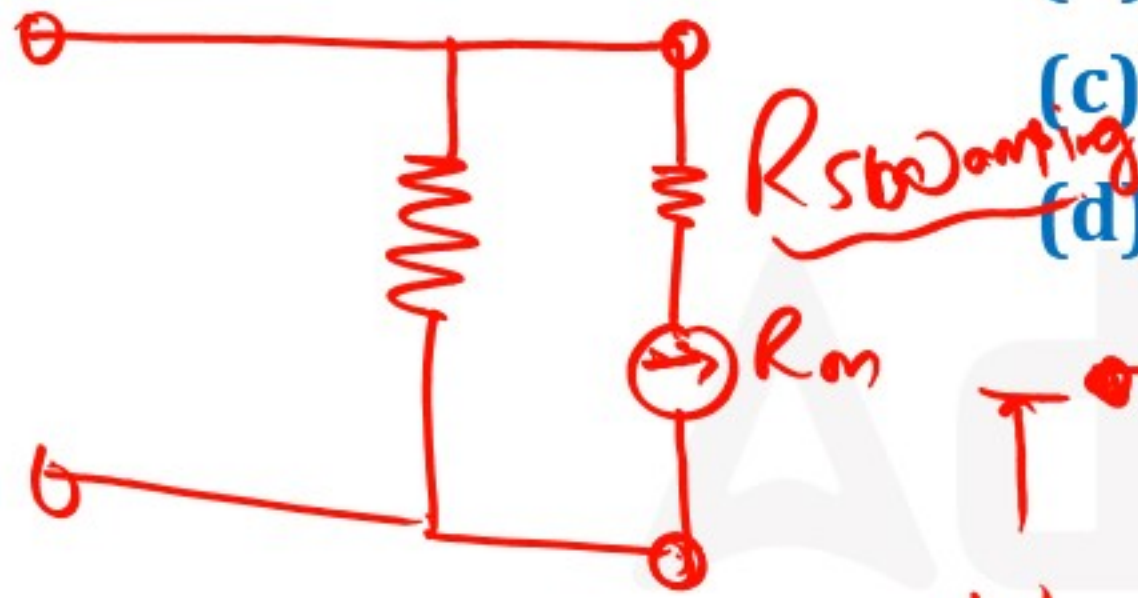(d) a high resistance is connected in parallel.





Q

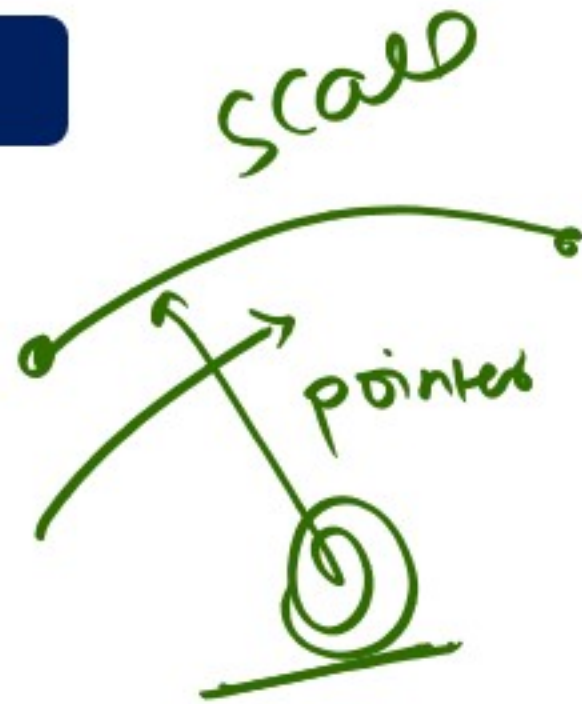


The controlling torque in gravity controlled meter is proportional to:

- (a)  $\cos \theta$
- (b)  $\sin \theta$
- (c)  $\tan \theta$
- (d) 0

$T_c$

Panel

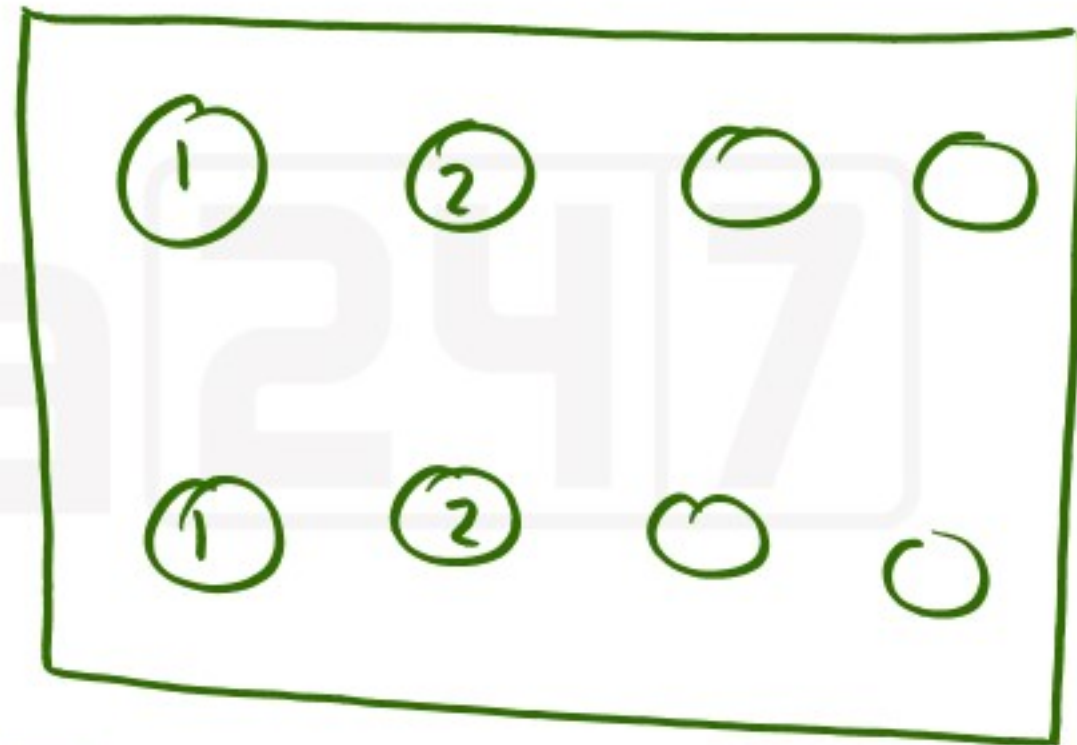

$T_c \propto \sin \theta$

$$T_c = WlS \sin \theta$$

Q

Swamping resistance is used to compensate error due to:

- (a) Stray magnetic field
- (b) Large supply voltage
- (c) Large supply frequency
- (d) Temperature variations

✓  $R_{swamp} \rightarrow \text{Temp. error}$

\* friction error



$$= \frac{T_{swamp}}{\text{weight}} \text{ (High)}$$



Q



With the decrease in the strength of the permanent magnet an insulation Megger due to ageing, the Megger reading will

- (a) be lower than actual.
- (b) be higher than actual.
- (c) remain unaffected.
- (d) fluctuate rapidly.

$$\phi \downarrow \quad E \downarrow$$

$$T_d \propto \phi I_a$$

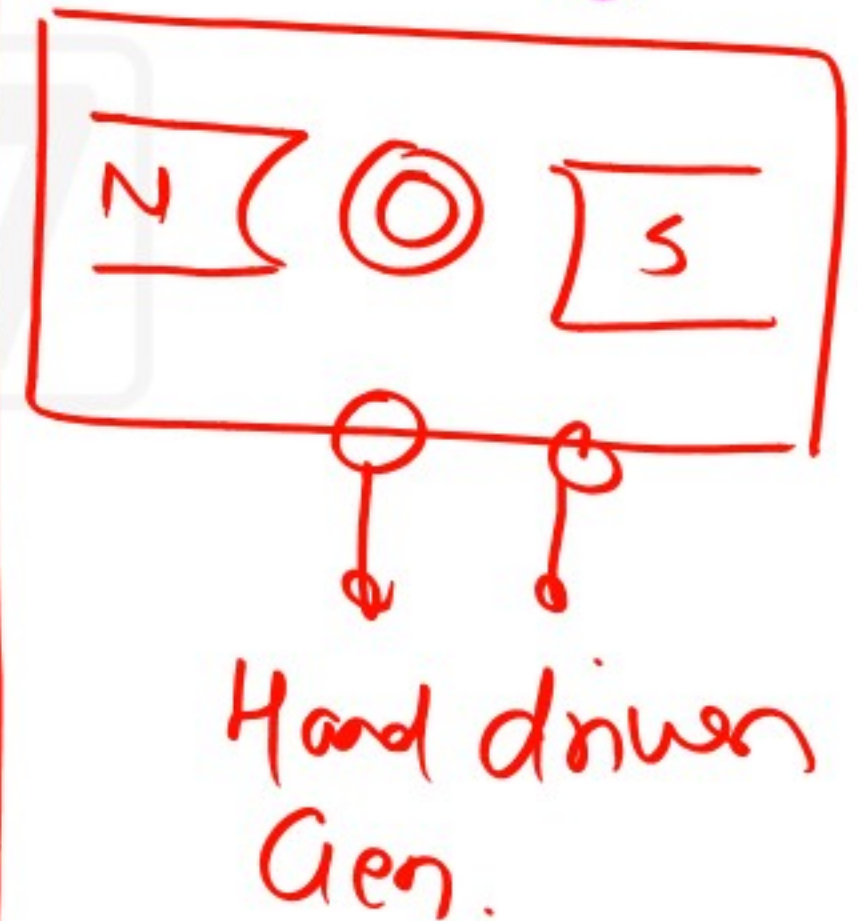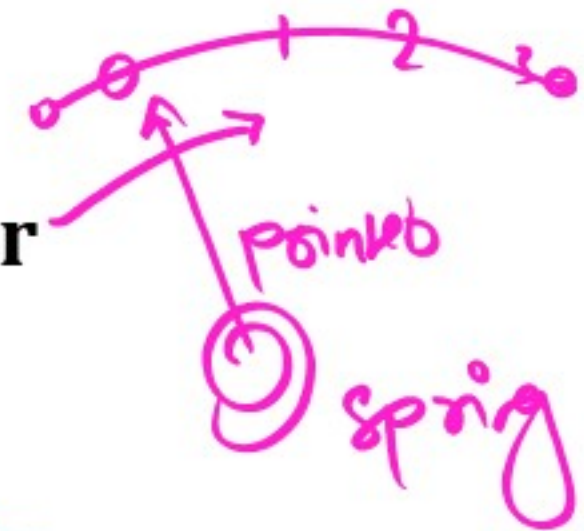
\* Megger  
 ↳ does Not  
 Required any  
 ext power  
 Source



Q

A static combination of control coil and compensating coil is used in Megger to minimize the effect of

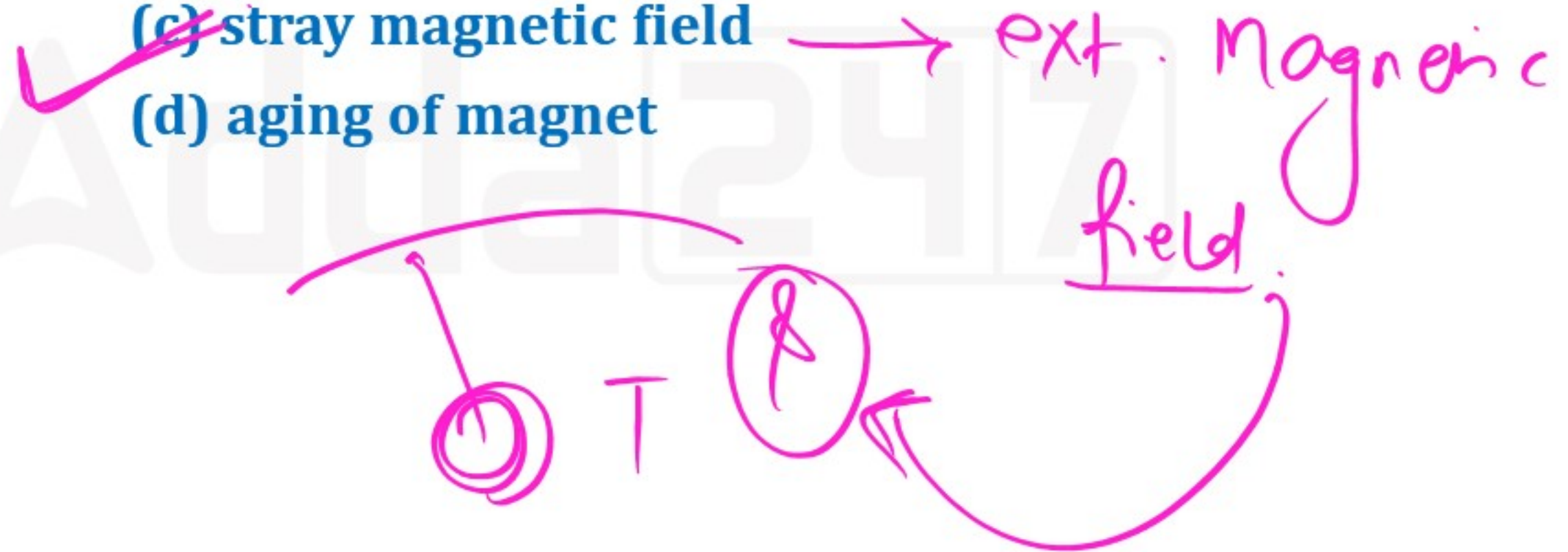- (a) stray capacitance
- (b) surface leakage
- (c) stray magnetic field
- (d) aging of magnet





Q

VVII

Match the items given in List - I and those in List - II (Temperature coefficient of Resistance). Select your answer using codes given in the lists:

List - I

(a) Aluminium

(b) Manganin

(c) Carbon

(a)  $a \rightarrow R, b \rightarrow Q, c \rightarrow P$ (b)  $a \rightarrow Q, b \rightarrow P, c \rightarrow R$ (c)  $a \rightarrow P, b \rightarrow Q, c \rightarrow R$ (d)  $a \rightarrow R, b \rightarrow P, c \rightarrow Q$ 

List - II

P. Negligibly small

Q. Positive

R. Negative

Al  $\rightarrow$  Conductors =  $\alpha^+$ Carbon  $\rightarrow$  S.M.  $\alpha^-$ 

$$\alpha = 0.0004$$

Q

The resistance of insulations, in general, \_\_\_\_\_ with temperature rise.

- (a) decreases
- (b) increases rapidly
- (c) increases slowly
- (d) does not change

Temp  
80°C

Temp ↑

R ↓

heat ↑

$\alpha^-$





Q


Determine the power (in W) delivered by the current source to the given electrical circuit.

By COR.

$$I_1 = \frac{5 \times 10}{10 + 3}$$

$$I_2 = \frac{5 \times 3}{13}$$

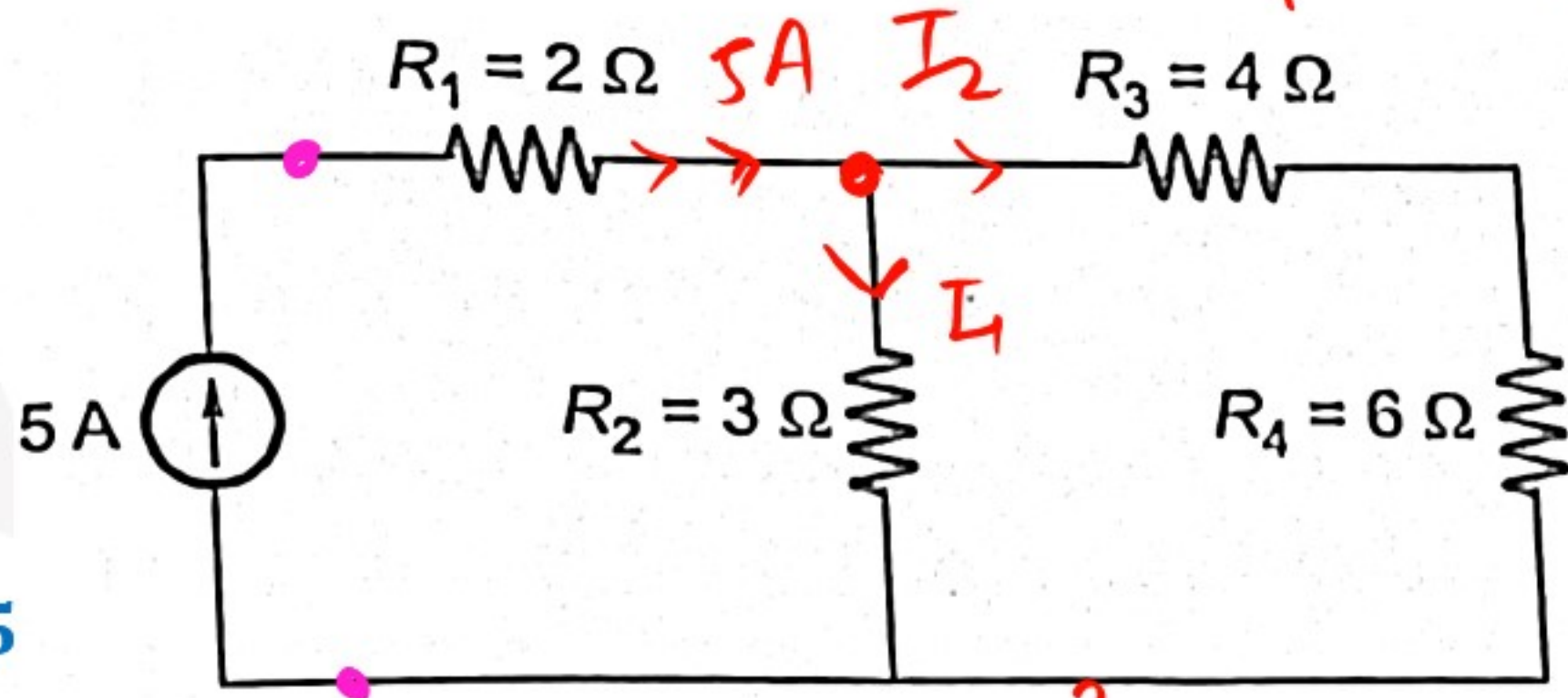(a) 92.5  
(b) 107.5  
(c) 104.2  
(d) 93.7



#  $P = VI$  |  $P = I^2 R_{eq}$

$$\# P = 5^2 \times 2 + I_1^2 \times 3 + I_2^2 \times 10$$





4433

**BILINGUAL**

# The Foundation SSC JE 2023

**Electrical**

नीव आपके सिलेक्शन का



**Start Feb 6, 2023** **9 AM to 6 PM**

**BILINGUAL**

## ELECTRICAL & ELECTRONICS ENGINEERING

### ka Mahapack

Live Class, Video Course  
Test Series, Ebooks

**At 3874 Only**

Q

SI unit of electrical energy is

(a) Watt - Second

(b) Joule

(c) kWh ✓

(d) Volt - Ampere - Second

Billing → Unit Consumption

$$E = P \times t$$

$$= \underline{\text{kWh}} \text{ (Common...)}$$



**Q**

Which of the following materials possesses the least resistivity?

- (a) Iron
- (b) Manganin
- (c) Aluminum
- (d) Copper

Adda247

Q

$$I = I_m \sin \omega t$$

A current of  $i = 6 + 10 \sin (100\pi t) + 20 \sin (200\pi t)$  is flowing through a series combination of a PMMC and moving iron instrument. Ratio of the two currents as registered by the M.I. and PMMC meter is MI/PMMC.

(a) 1.81

(b) 3.11

(c) 2.82

(d) 2.63

$$i = \underbrace{6}_{\text{dc}} + \underbrace{10 \sin(100\pi t)}_{\text{AC}} + \underbrace{20 \sin(200\pi t)}_{\text{AC}}$$

PMMC = GA  
Reading

$$I_{m.o.I} = \sqrt{6^2 + \left(\frac{10}{\sqrt{2}}\right)^2 + \left(\frac{20}{\sqrt{2}}\right)^2}$$

$$= \sqrt{6 + 50 + 200}$$

\* PMMC - only

dc

\* M.I. = A.C. +

dc

↳ effective (RMS)



Q


An ac meter of resistance  $R_m$  and reactance  $X_m$  is connected in series with a resistance  $R_s$ . A shunt of impedance  $(R_{sh} + jX_{sh})$  is applied in parallel to the existing combination of meter and  $R_s$ . The current division across the two branches will be independent of frequency

when

$$* I_m = \frac{V}{Z}$$

$$Z = R + jX$$

$$X_L = 2\pi fL$$

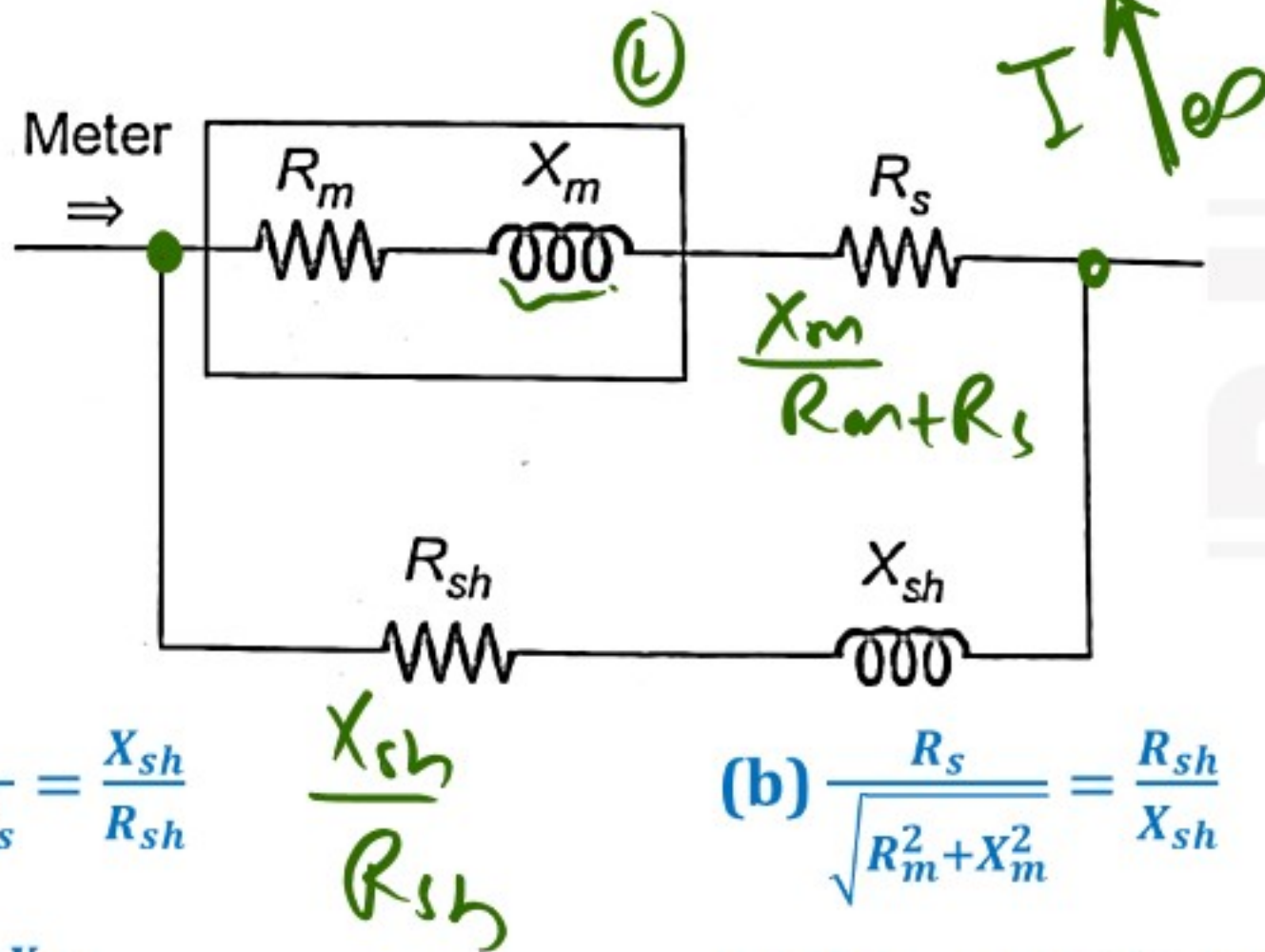

\* Meter Reading is independent of temp. if meter T.C & shunt T.C are equal.

$$\# \tau = \frac{L_1}{R_1} = \frac{X_{L1}}{R_{11}}$$

$$(a) \frac{X_m}{R_m + R_s} = \frac{X_{sh}}{R_{sh}}$$


$$\frac{X_{sh}}{R_{sh}}$$

$$(b) \frac{R_s}{\sqrt{R_m^2 + X_m^2}} = \frac{R_{sh}}{X_{sh}}$$

$$(c) \frac{X_m}{R_m} = \frac{X_{sh}}{R_{sh}}$$

$$(d) (R_s + R_m)^2 + X_m^2 = R_{sh}^2 + X_{sh}^2$$

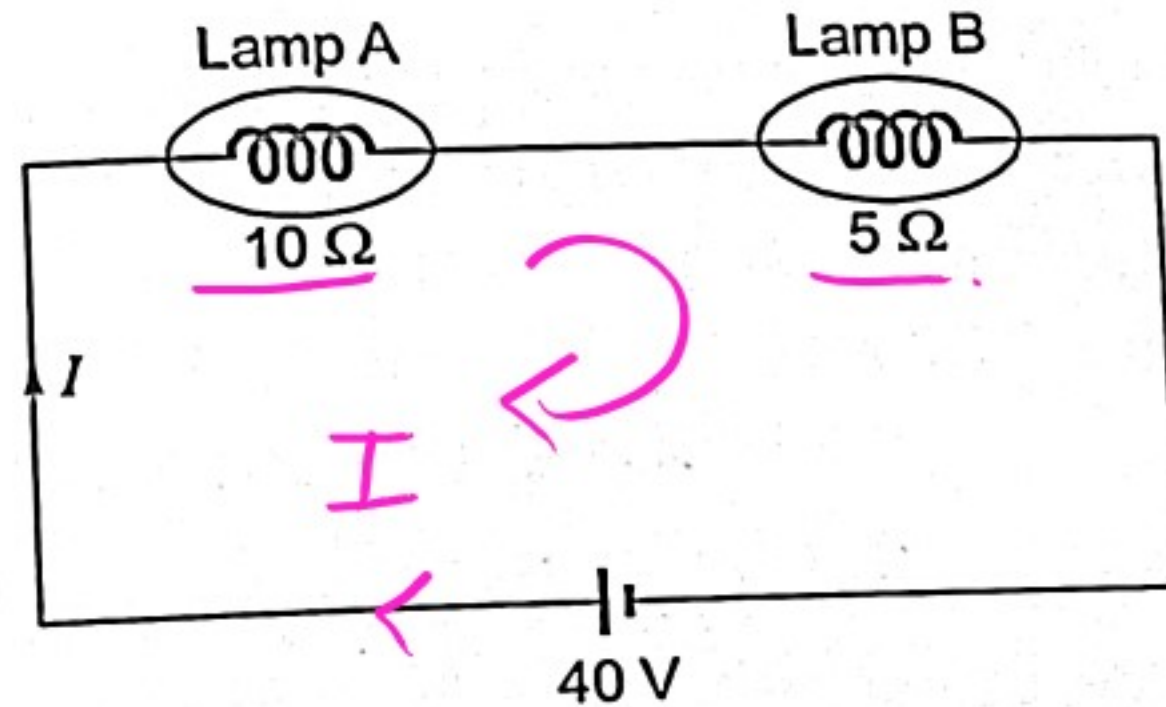**Q** Determine the power (in W) of lamp A and lamp B respectively for the given circuit diagram.



- (a) 75.56, 33.86
- (b) 76.65, 38.86
- (c) 70.76, 35.37
- (d) 68.62, 38.86

$$I = \frac{40}{15} = \frac{8}{3} \text{ Amp}$$

$$P_a = \frac{64 \times 10}{9}$$

$$P_b = \frac{64 \times 5}{9}$$



**Q** Which one of the following statement is TRUE?

(a) Superposition theorem is not applicable for voltage calculation.

(b) Superposition theorem is not applicable for power calculation.

(c) Superposition theorem is not applicable for bilateral elements.

(d) Superposition theorem is not applicable for passive elements.

SPT  
Circuit

SPT  
Ckt  $\rightarrow$  Linear  
Homogeneity Add

Q


Which one of the following is an active element in a circuit?

- (a) Capacitor
- (b) Resistance
- (c) Inductor
- (d) Current source

\* Neg. Impedance is

The concept of only

Active only.

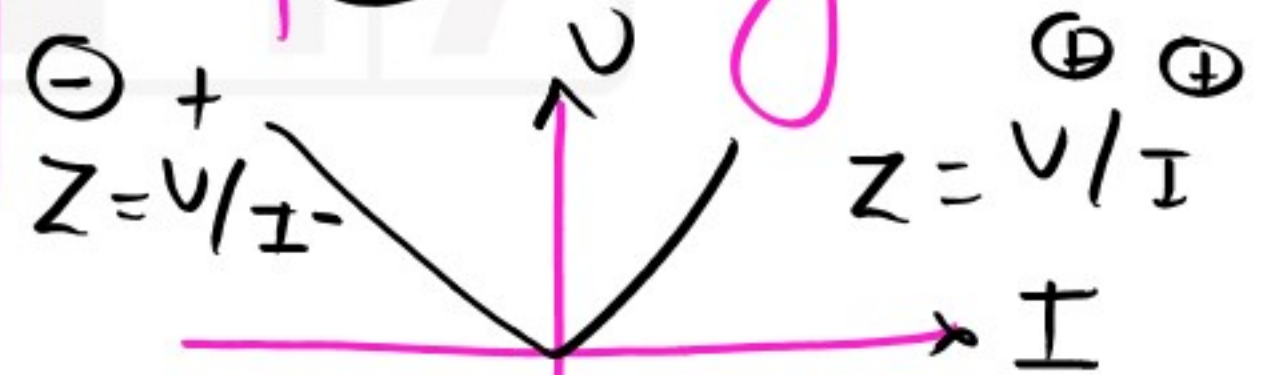


Active



Determine the Thevenin's equivalent resistance (in ohms) across terminals  $x$  and  $y$  for the given electrical circuit.

Q

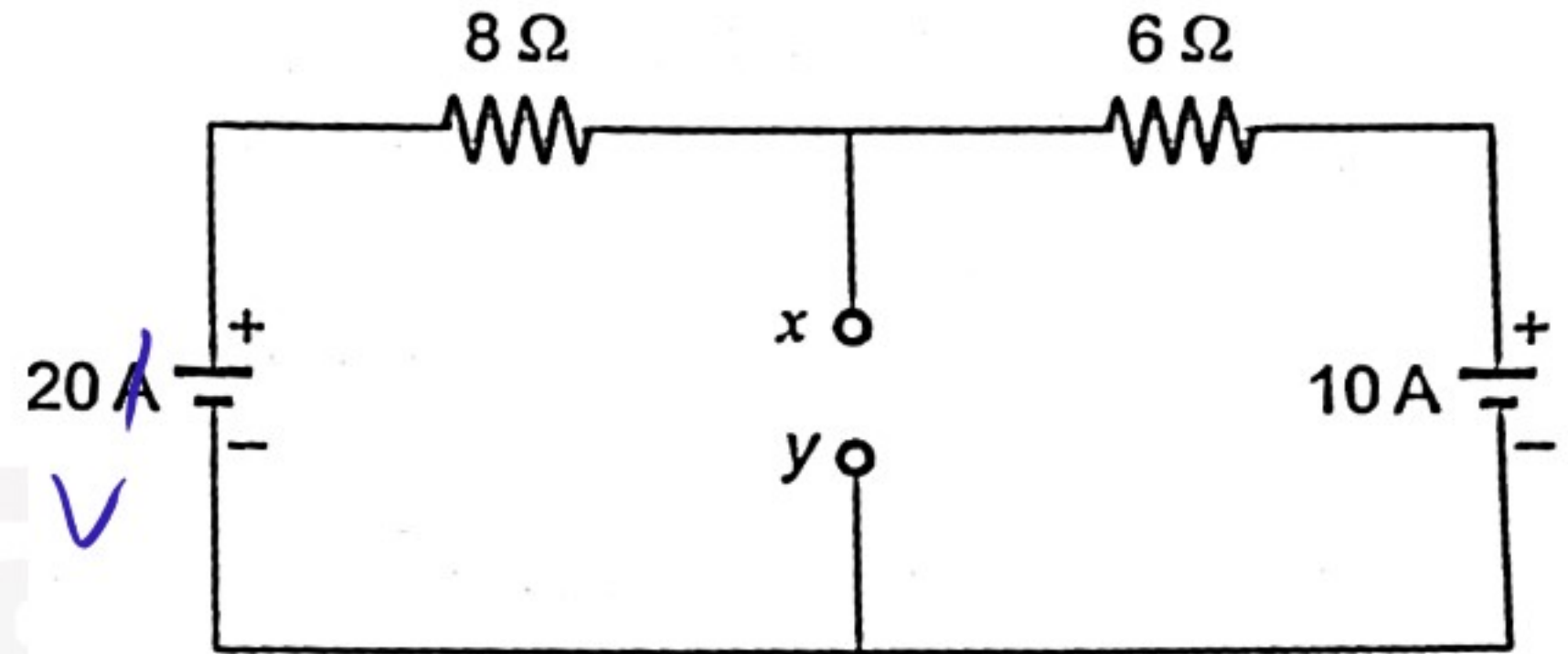


- (a) 1.21  
 (b) 2.32  
 (c) 3.43  
 (d) 4.45

$$R_{th} = \frac{6 \times 8}{6 + 8} = \frac{48}{14}$$

Q

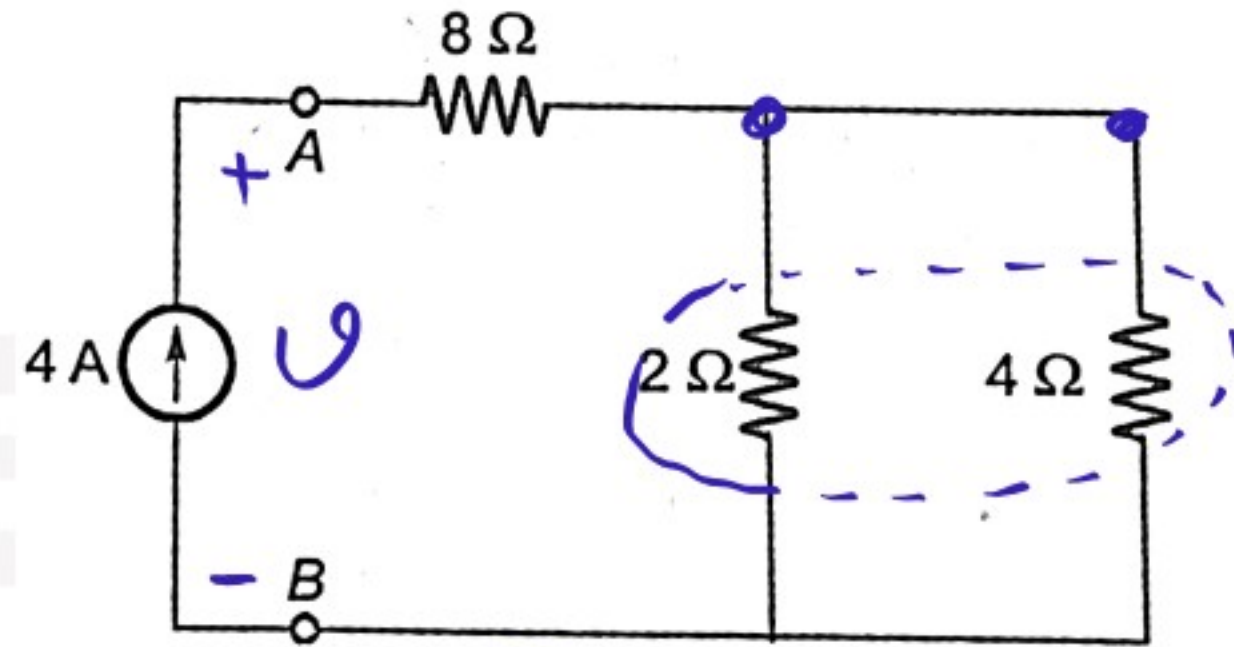What will be the voltage (in V) between points 'A' and 'B' in the given electrical circuit?



- (a) 38.25  
 (b) 37.32  
 (c) 36.62  
 (d) 32.24

$$V = 8 \times 4 + \frac{8}{6} \times 4$$

$$= 32 + \frac{32}{6}$$



Q

The open - circuit voltage across the load is equal to 45 V. Calculate the load voltage (in V) when the maximum power is transferred to the circuit.


(a) 11.25

(b) 22.5

(c) 45

(d) 90


$$V = 45 \cdot \frac{1}{2}$$

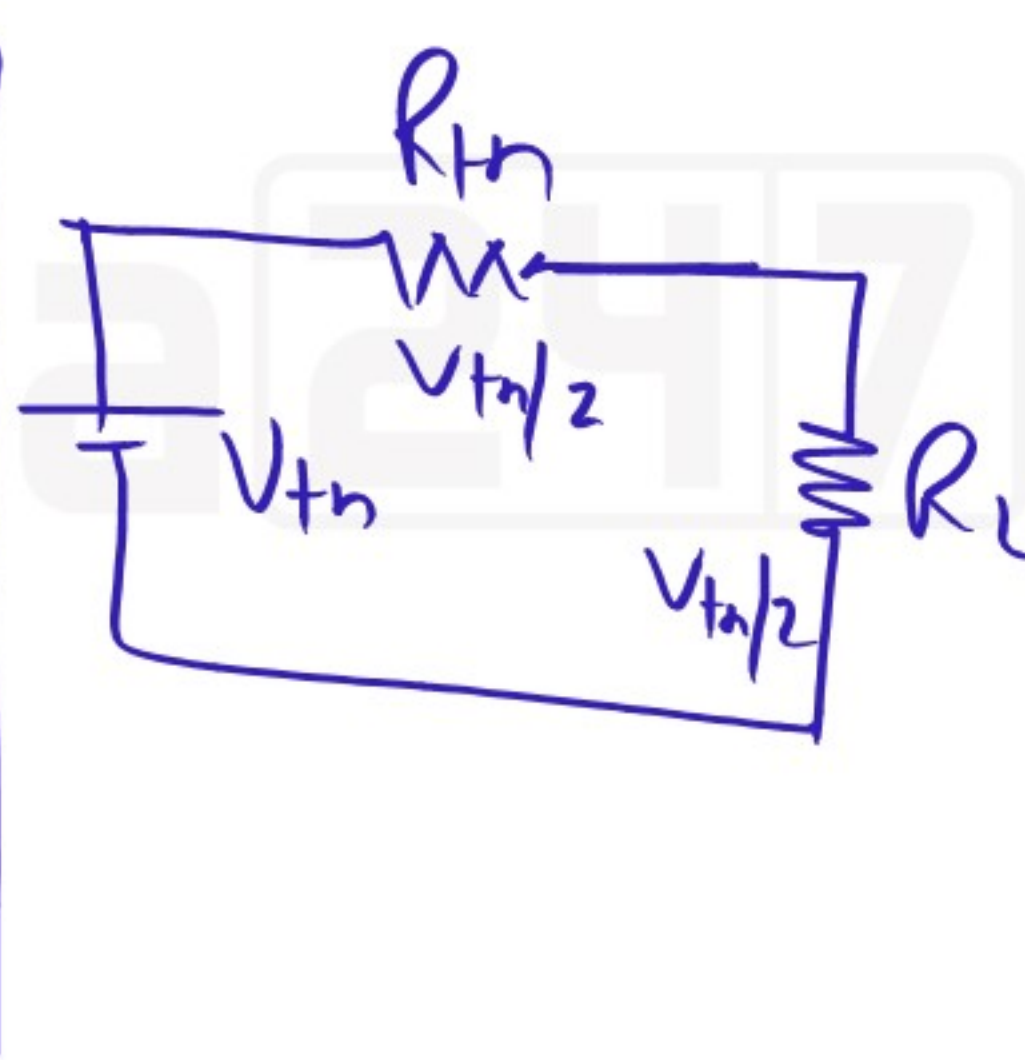

MPT  
 $R_L = R_{th}$

Q

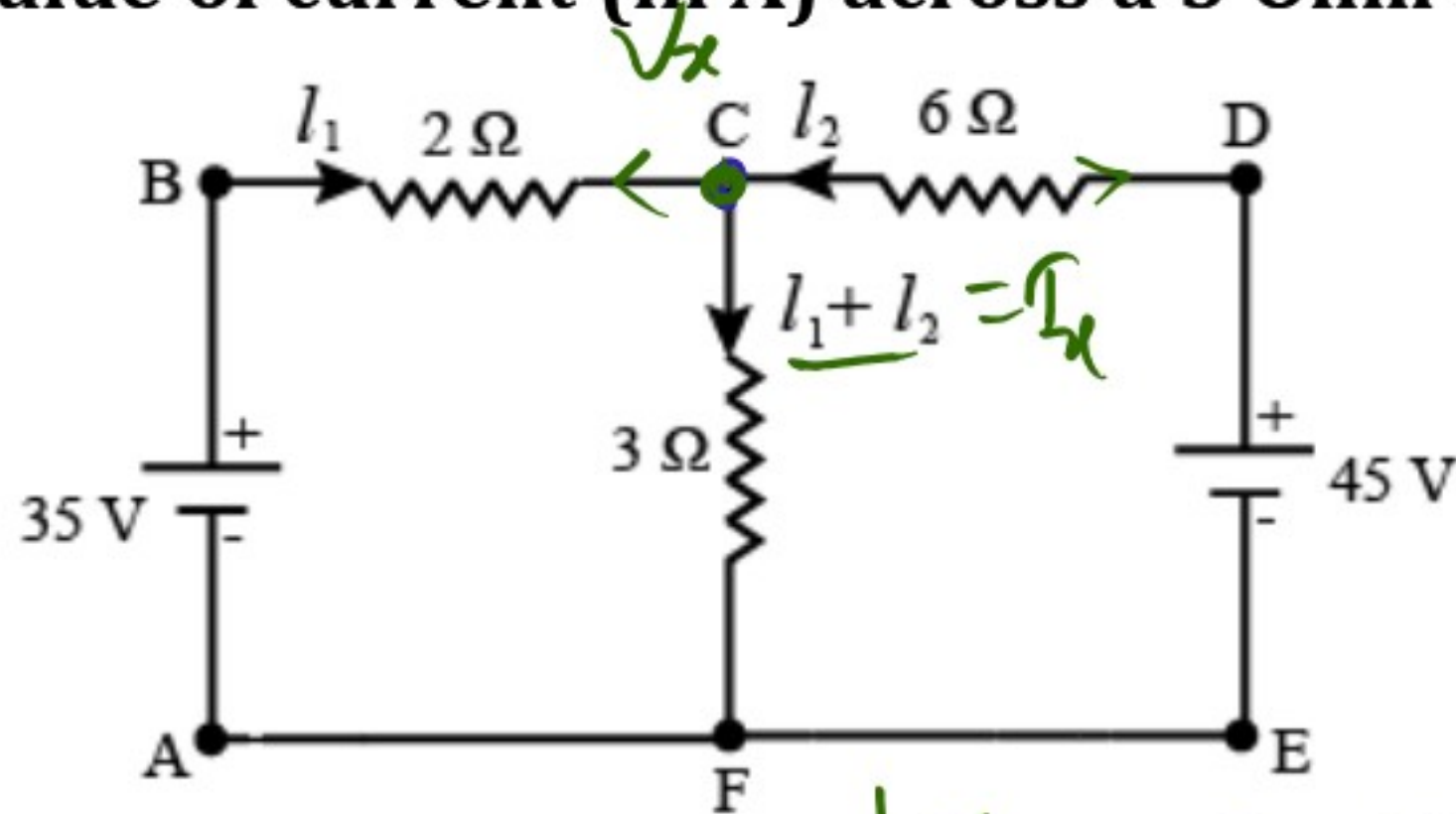Find the value of current (in A) across a 3 Ohm resistance



(a) 5.5

(b) 7.3

(c) 6.5

~~(d) 8.3~~

By Nodal.

$$\frac{V_x - 35}{2} + \frac{V_x}{2} + \frac{V_x - 45}{6} = 0$$

$$V_x = 25$$


$$I_x = \frac{V_x}{3}$$

$$I_x = \frac{25}{3}$$



Q

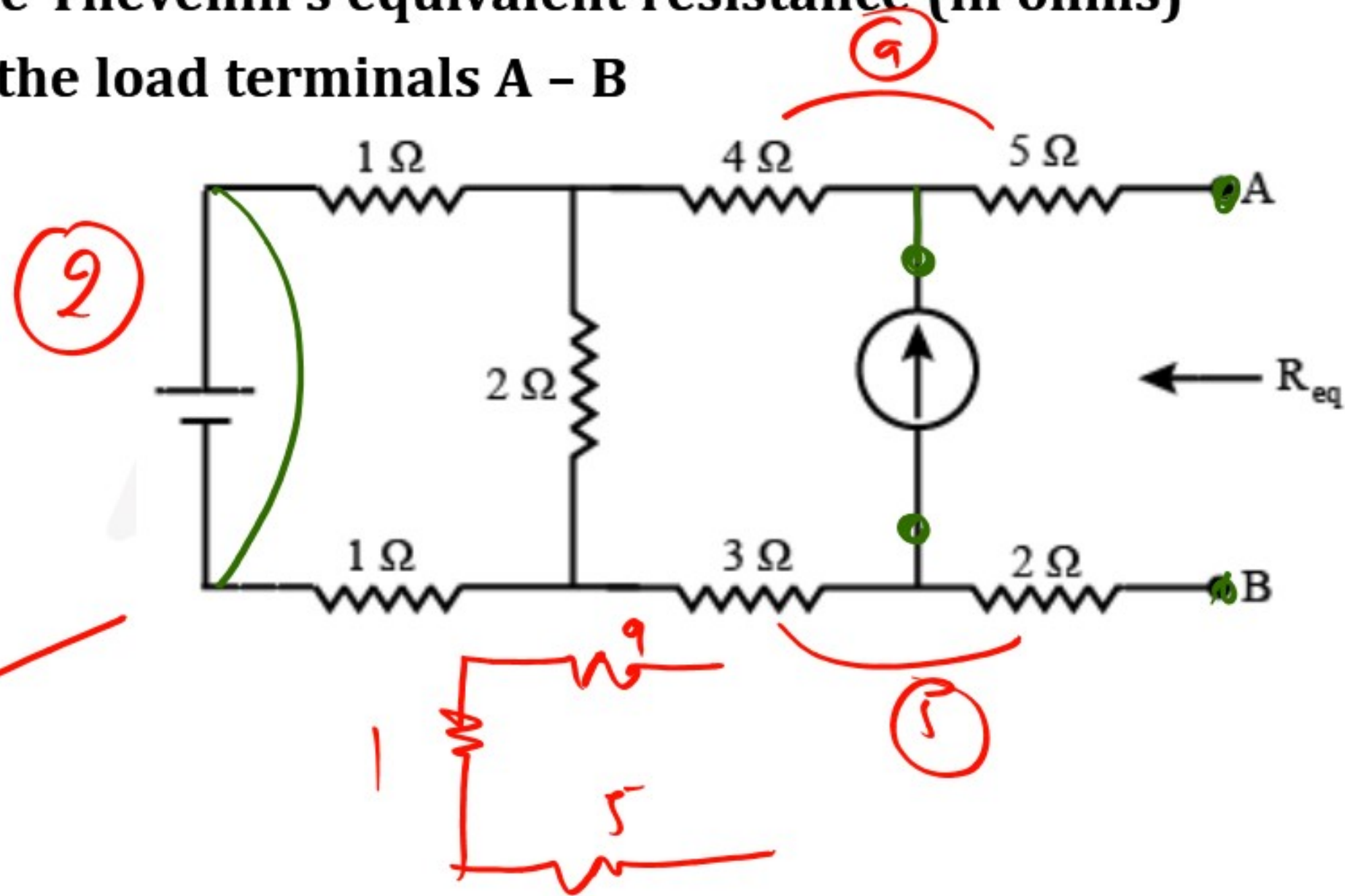Find the Thevenin's equivalent resistance (in ohms) across the load terminals A - B



(a) 10

(b) 15

(c) 20

(d) 25

Determine the percentage (in %) of maximum power delivered to the load resistance, when  $R_L = 3R_{Th}$ .

Q

$$R_L = R_{Th}$$

~~$$\eta = 50\%$$~~

$$R_L = nR_{Th}$$

(a) 50

(b) 65

(c) 70

(d) 75

$$P = I^2 \cdot R_L$$

$$I = \frac{V_{Th}}{R_L + R_{Th}}$$

$$R_L = 3R_{Th}$$

$$R_L = 3R_{Th}$$


$$P = \frac{V_{Th}^2}{4R_{Th}} \times \frac{3}{4}$$

$$P_{max} = 75\%$$




For the circuit shown below, find the current (in A) produced by the 50 V battery

Q

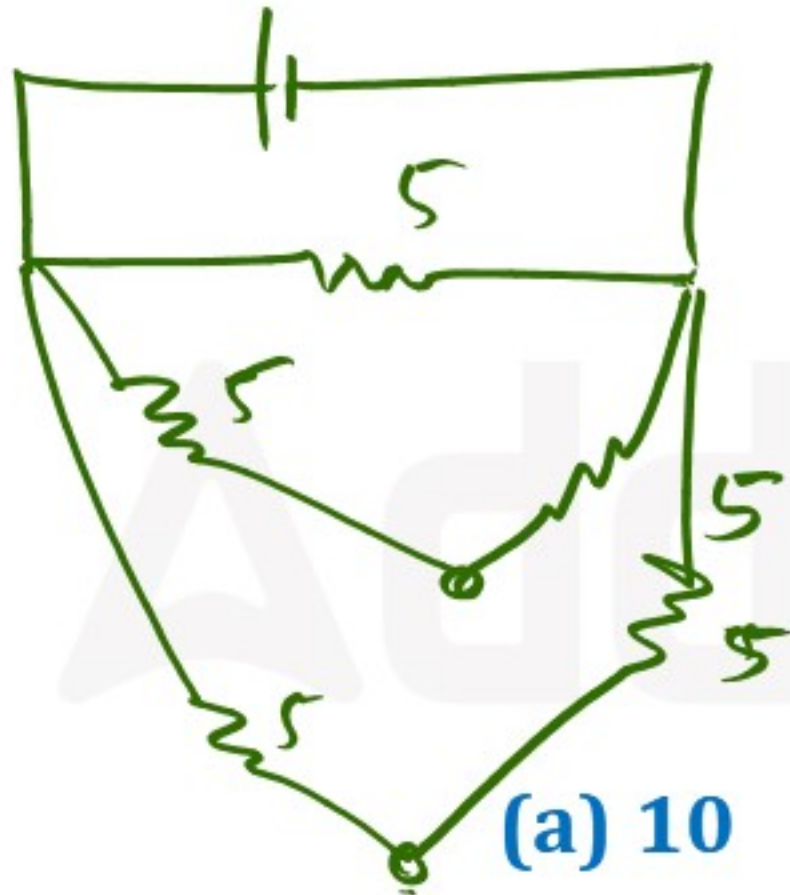

- (a) 10      (b) 20  
(c) 30      (d) 40

$$R_{eq} = 2.5 \Omega$$

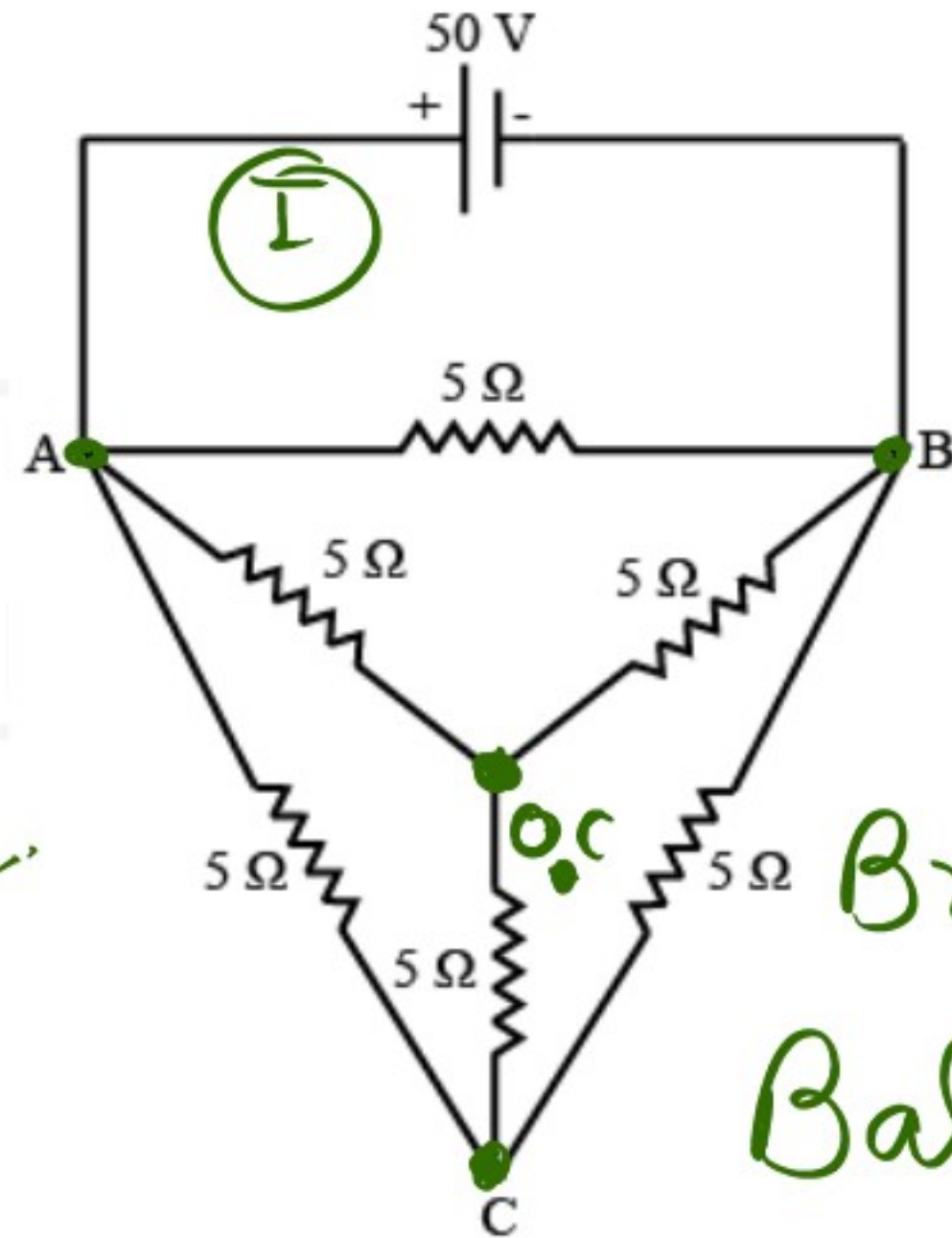

$$I = \frac{V}{R_{eq}}$$

$$I = \frac{50}{20}$$



Bridge is  
Balanced.

Q

Which of the following circuits can be used as series to parallel converter?

- (a) ~~De-multiplexer~~  
 (b) encoder  
 (c) decoder  
 (d) multiplexer

एक ही  
जगह

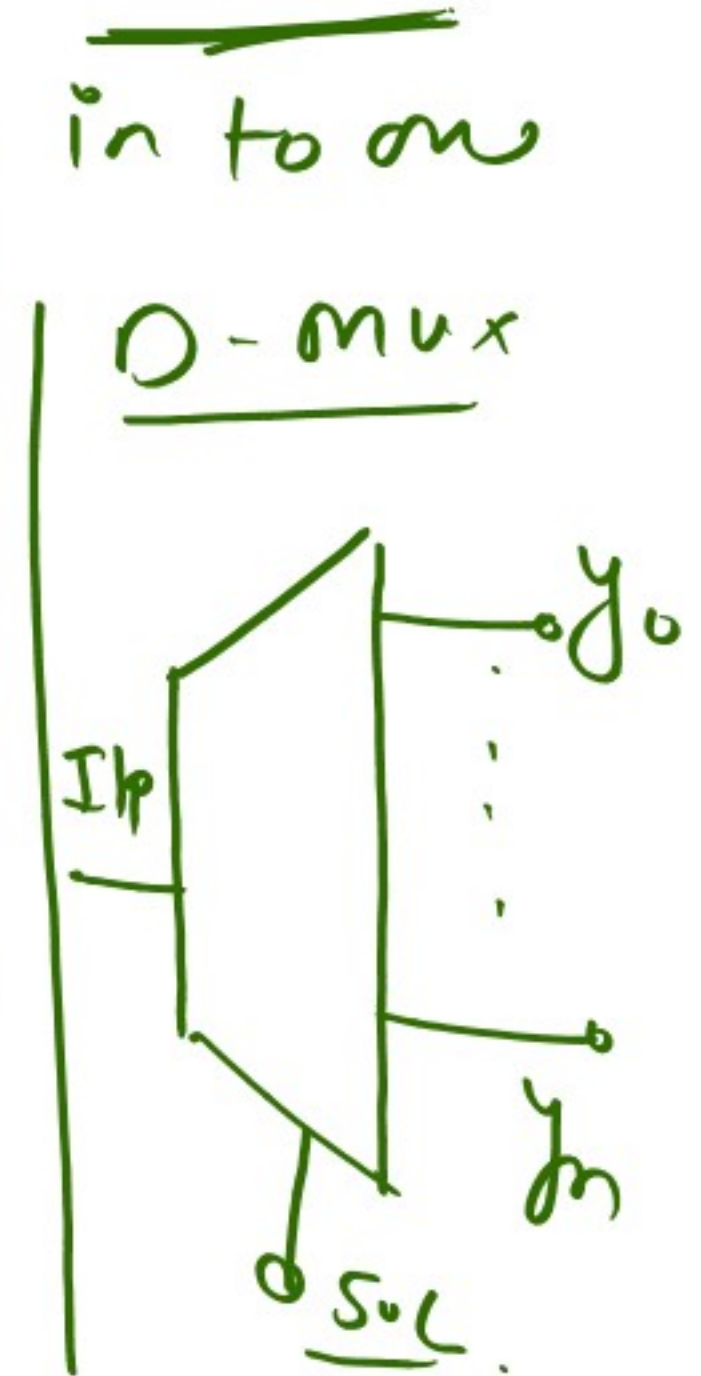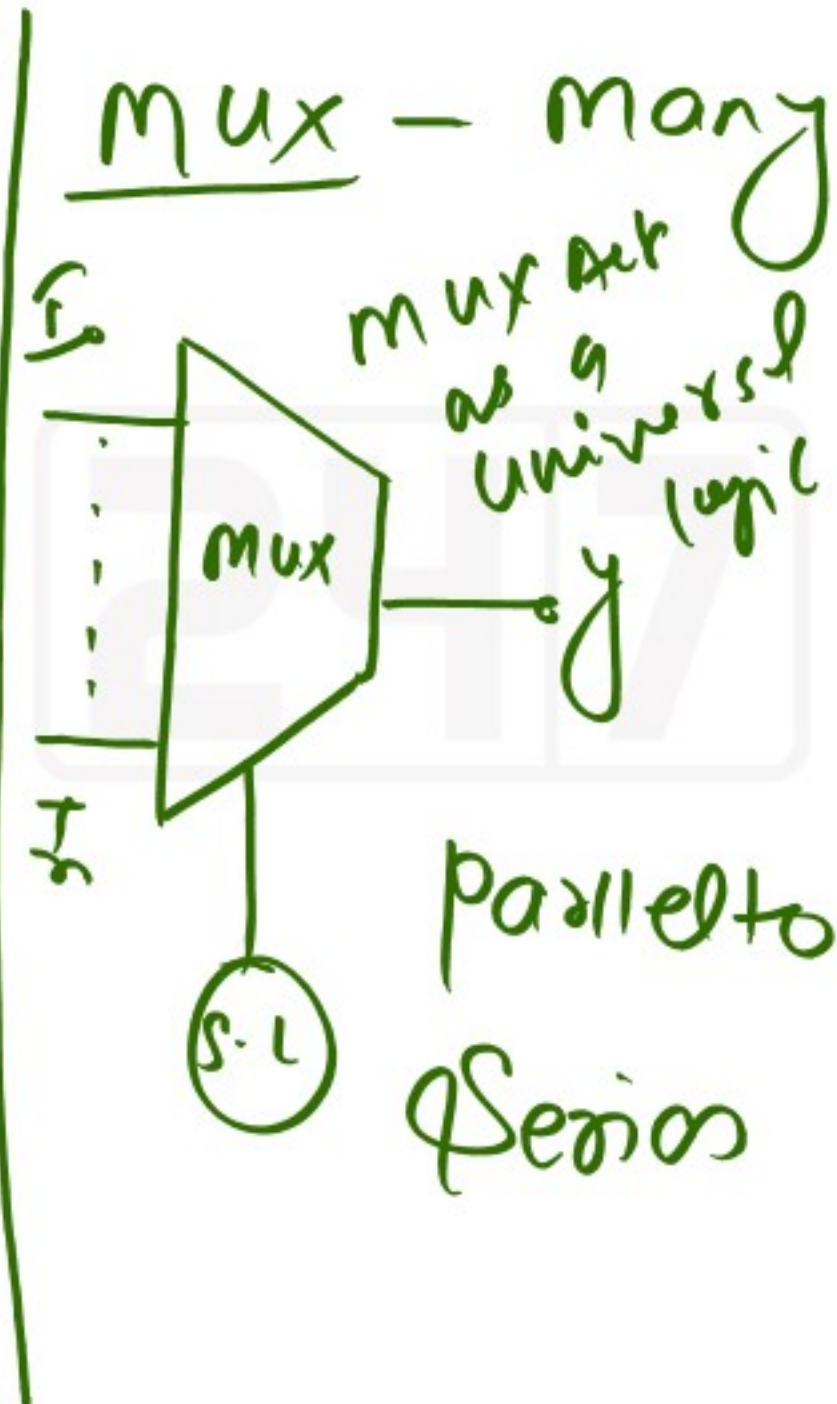



Q


For all possible input combinations, the exact reverse output of AND gate can be obtained by \_\_\_\_\_ gate.

(a) EX - OR

(b) NAND

(c) NOR

(d) NOT

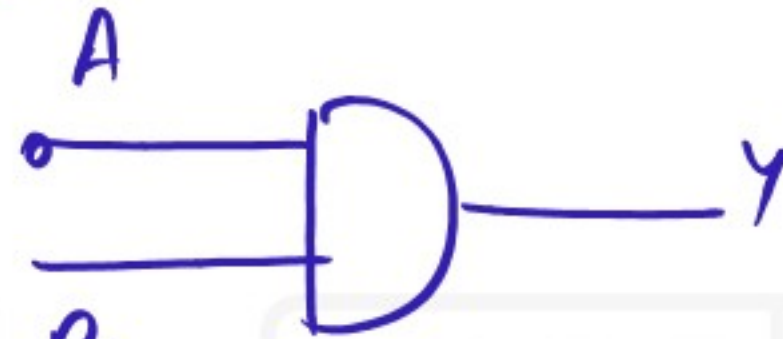

$$Y = A \cdot B$$

$$Y = 0 \cdot 0$$


$$Y = 0$$

NAND Gate

$$Y = \overline{A \cdot B} = \overline{A} + \overline{B}$$
$$= \overline{0} + \overline{0}$$
$$= 1$$

Q

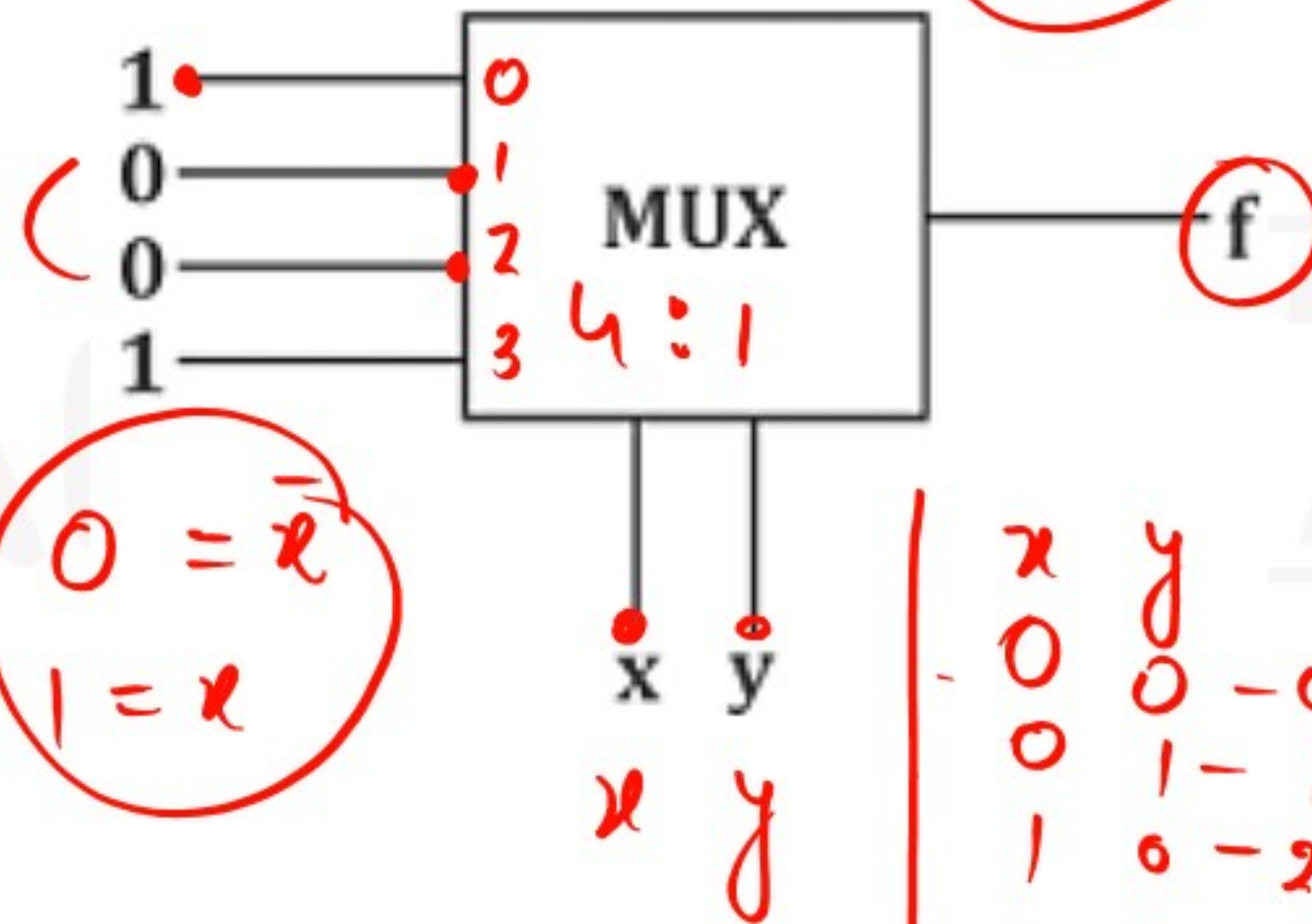What is the output  $f(x, y)$  of the multiplexer resulting from the input logical values?



- (a) XNOR gate  
 (b) XOR gate  
 (c) NOR gate  
 (d) AND gate

$$f = \bar{x}\bar{y} \cdot 1 + 0 + 0 + xy \cdot 1$$

$$f = \bar{x}\bar{y} + xy$$

$$= x \odot y$$



Q

The resolution of a 10 - bit D/A converter is given by

(a)  $\frac{1}{1023}$

(b)  $\frac{1}{1024}$

(c) 1023

(d) 1024

$$\text{Res.} = \frac{1}{2^n - 1}$$

$$n = \text{No. of Bits}$$

$$\text{Res} = \frac{1}{2^{10} - 1}$$

$$\text{Res} = \frac{1}{1024 - 1}$$

$$= \frac{1}{1023}$$

Q

The number of unused states in a 3 - bit Johnson counter is -


- (a) 8  
(b) 12  
(c) 3  
(d) 2

Ring

Johnson

\* Counter's

Sy. Asy  
any seq. Up or down  
seq.

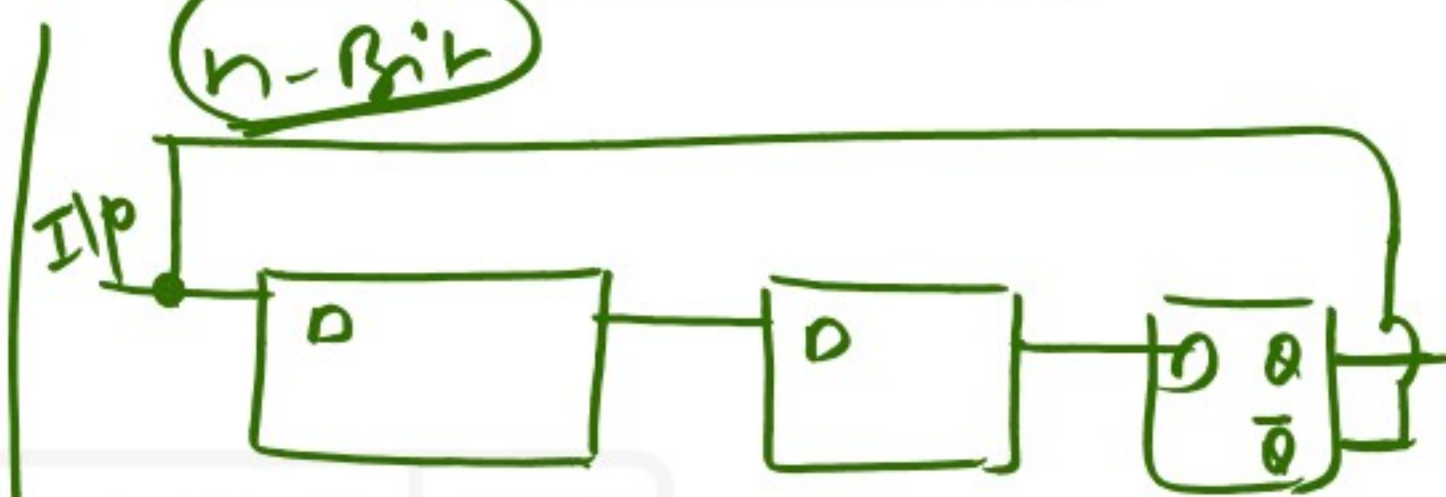

→ 0000  
→ 1000  
→ 0100  
~ ~ ~

\* Unused state

$$= 2^n - 2n$$

$$= 8 - 6 = 2$$

\* Used state

$$= 2n = 6$$



\* total =  $2^n$



The initial contents of the 4 - bit series - in - parallel out, right shift, shift register as shown in figure below are 1010 after 3 clock pulses the contents of the contents of the shift register will be

0  
Imp

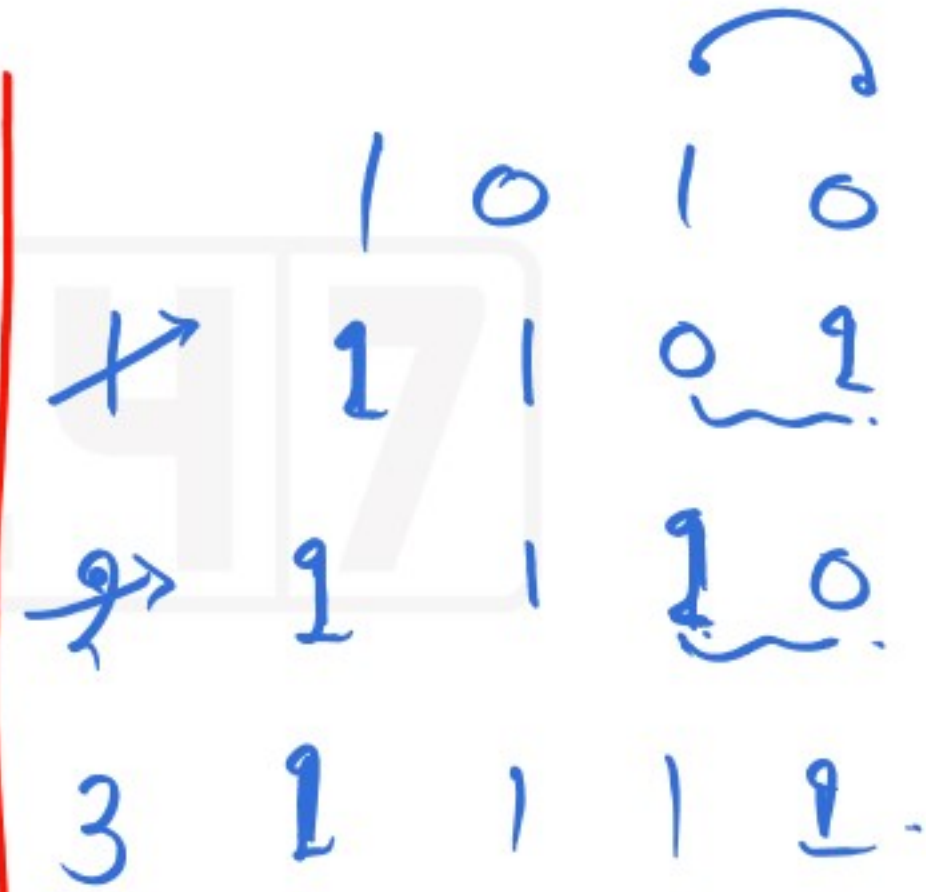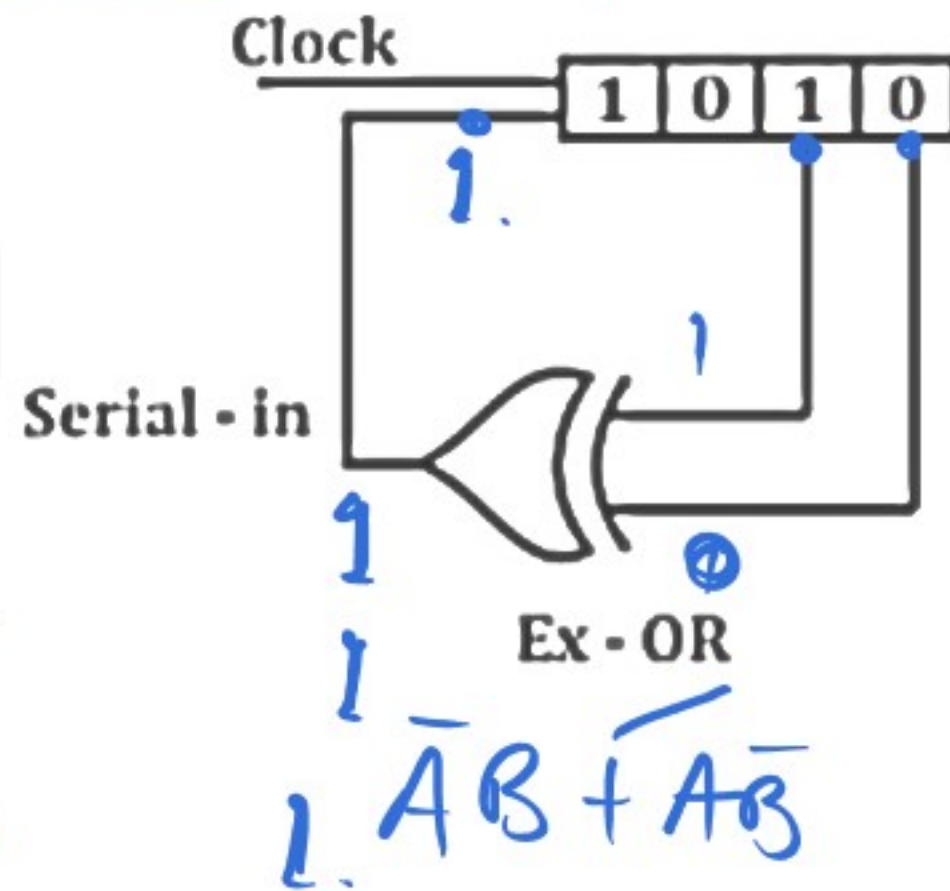- (a) 1111  
(b) 1101  
(c) 1110  
(d) 1010



$$f_{in} = f, f_o = f/2$$

Q

The figure of merit of a logic family is given by \_\_\_\_\_


- (a) fan out  $\times$  propagation delay time
- (b) Noise margin  $\times$  power dissipation
- (c) Propagation delay time  $\times$  power dissipation
- (d) gain  $\times$  bandwidth

\* fastest  
logic family

= ECL

$$fom = t_{pd} \times P_d$$

$T_{on}$  or  $T_{off} = low$

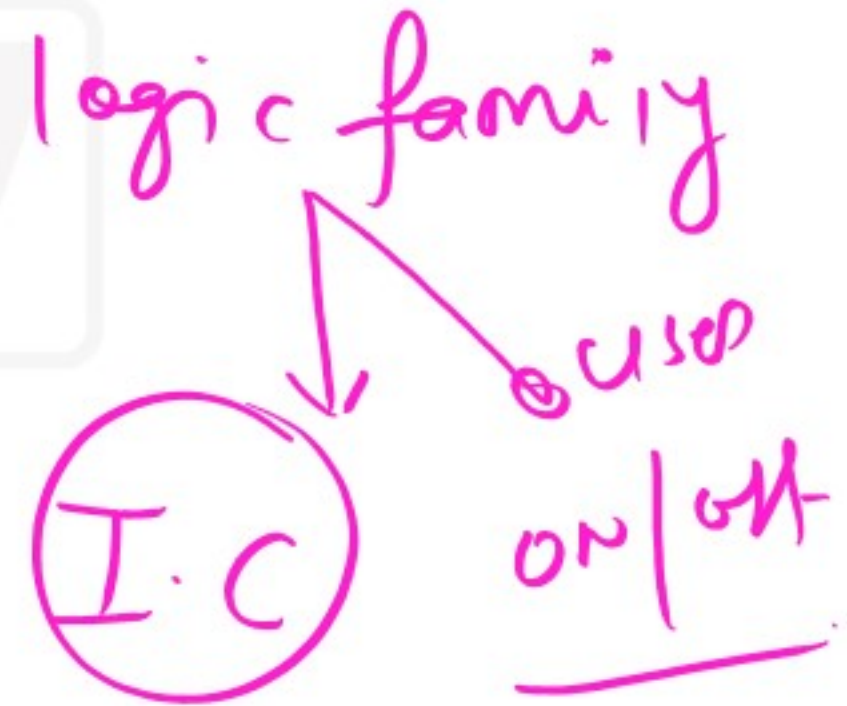




Q

Sol. In N-P-N transistor, emitter current is

- (a) Slightly less than collector current  
 (b) Slightly more than collector current  
 (c) equal to collector current  
 (d) equal to base current

→ power

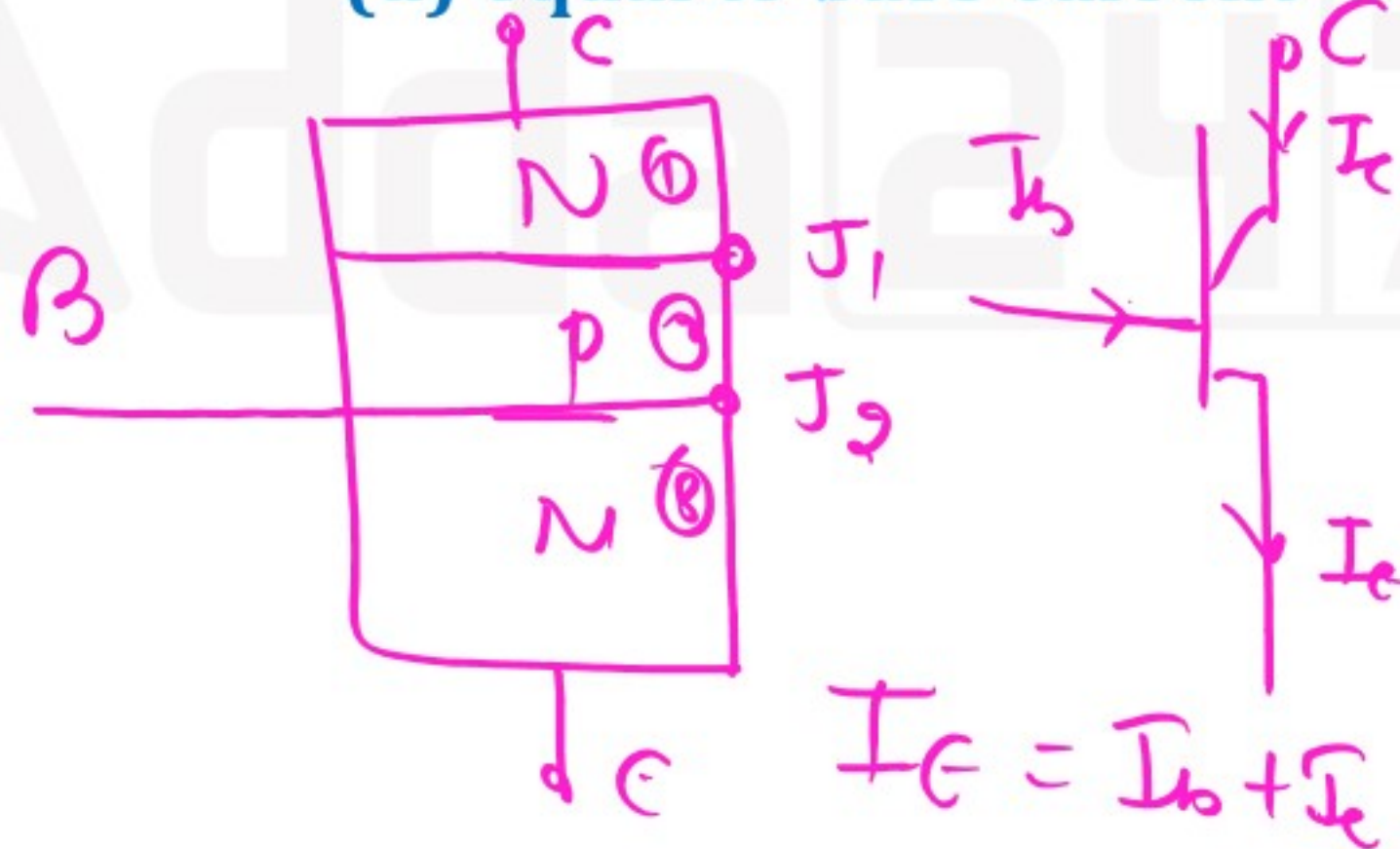

$I_b =$  Continuous  
to turned  
on

E, E = main


B = Control.

Consider the following statements:



A clamper circuit

1. Amplifies the waveform
2. Adds or subtracts a dc voltage to or from a wave form
3. Does not change the shape of the waveform which of the statements given above are correct?


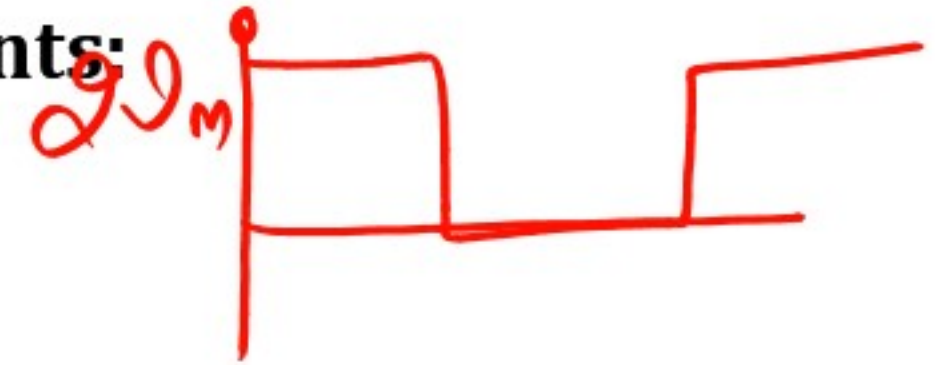
- (a) 1 and 2
- (b) 2 and 3
- (c) 1 and 3
- (d) 1, 2 and 3



Clamper ckt  
↓  
to store dc

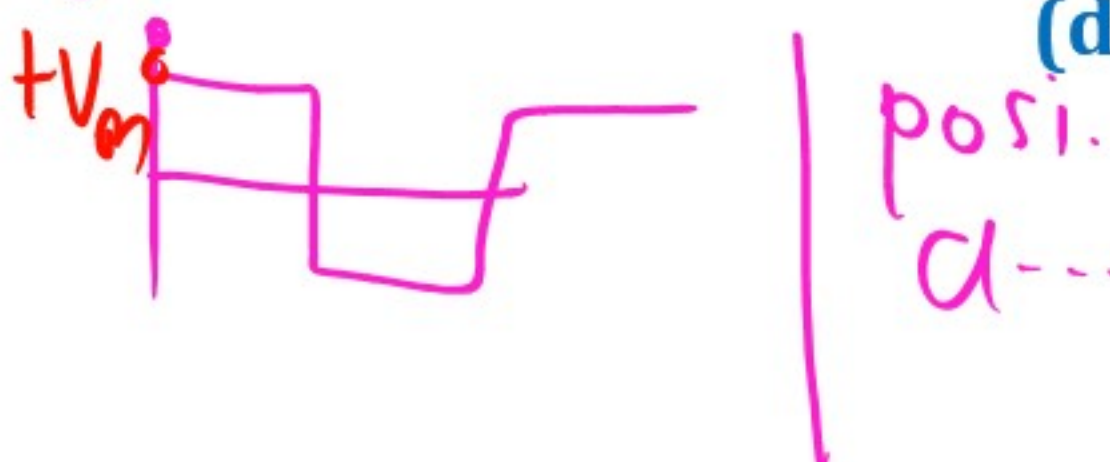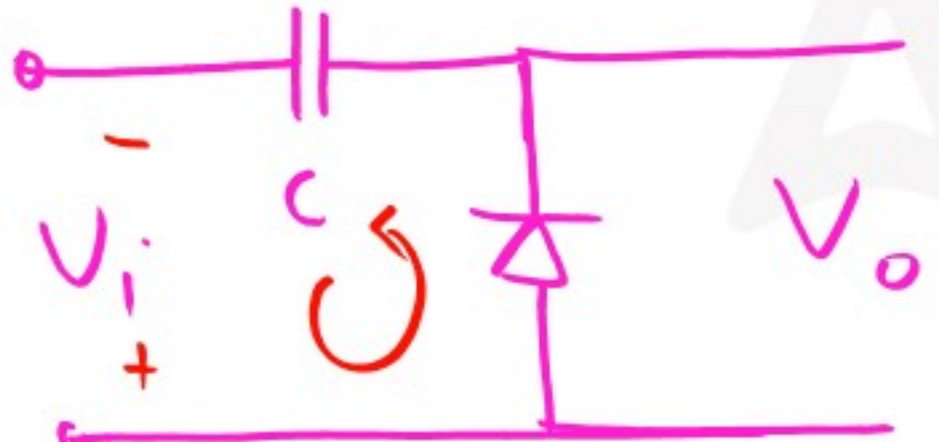

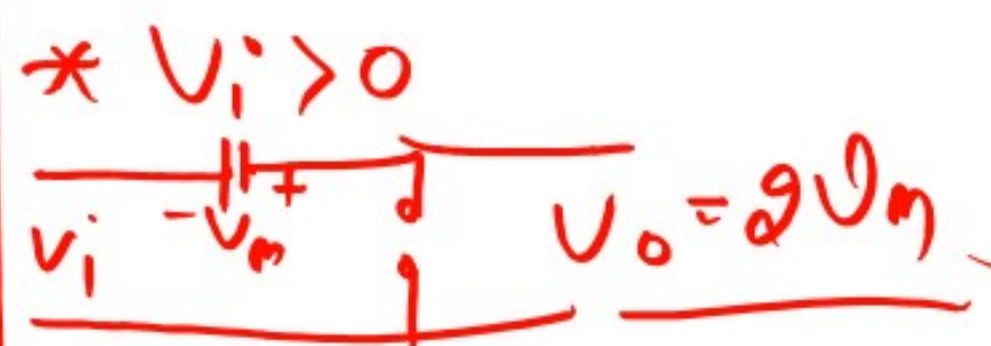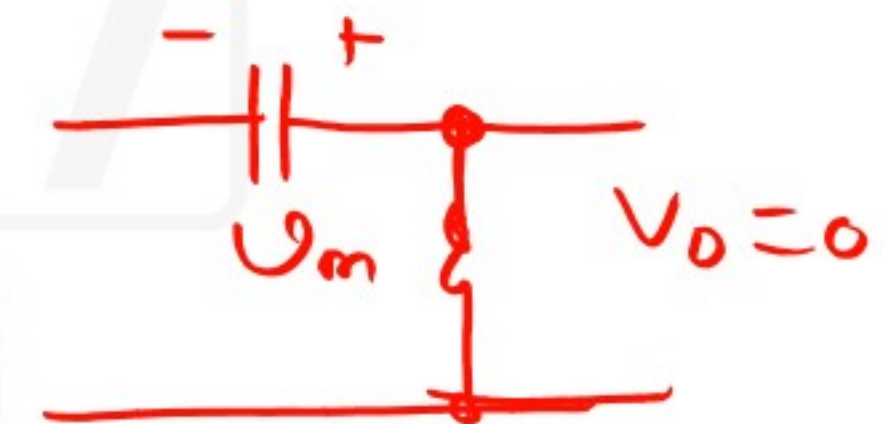
$V_i < 0$   
 $d \rightarrow$  FB,  
 $C \rightarrow$  start charging





Q

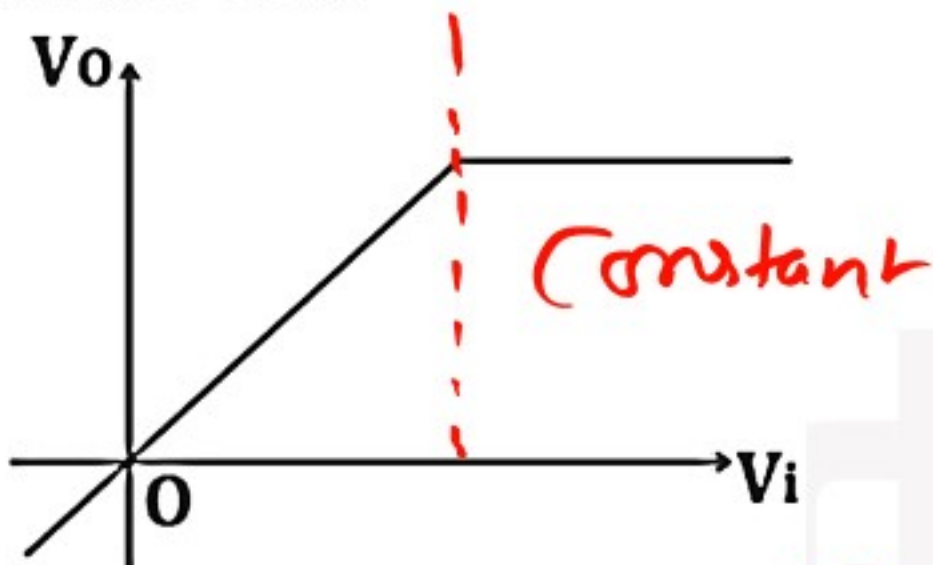
The voltage transfer characteristic as shown in the figure will relate to a



1. Full wave rectifier
2. Half wave rectifier
3. Voltage regulator

Which of the above is/are correct?

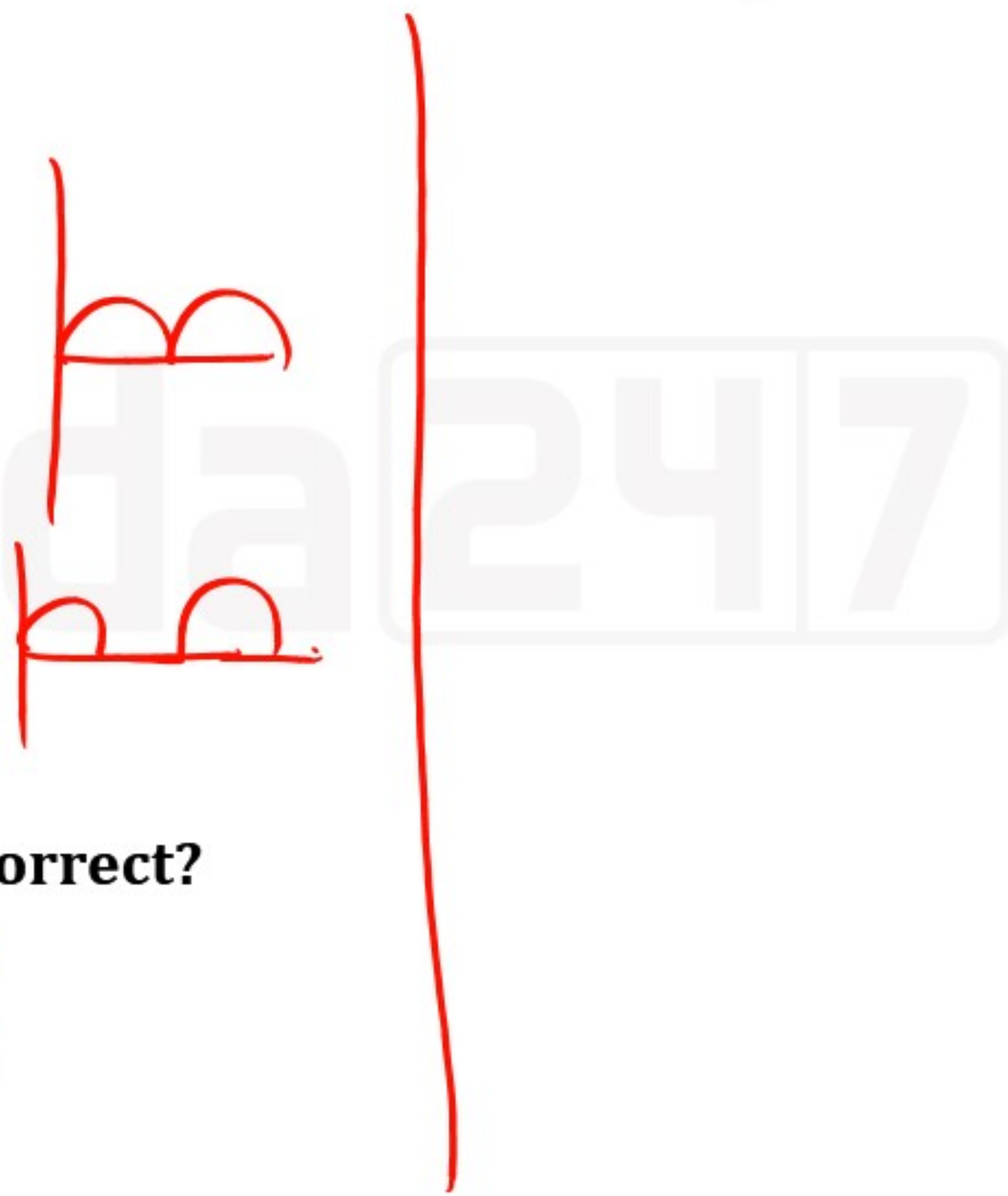- (a) 1 and 2                      (b) only 1  
(c) only 2                        (d) only 3



Q

Which transistor configuration is most suitable for impedance matching.

- (a) CE configuration
- (b) CB configuration
- ✓ (c) CC configuration
- (d) CE and CB both

\* Impedance matching  
↳ MPT  
 $Z_L = Z_S$

\* Common Collector

$$A_v = \text{unity}$$

$$\underline{V_o \propto V_i}$$



Q

A rectifier which has ripple factor of 0.482 and power conversion efficiency equal to 81.2%. the rectifier is

Ripple factor = \_\_\_\_\_  
 Harmonics

$$R.f = \sqrt{ff^2 - 1}$$

$$ff = \frac{V_{rms}}{V_0}$$

1. full wave (non-bridge) rectifier ✓
2. Half wave rectifier
3. bridge rectifier

Which of these are correct?

- (a) 1 and 2
- (b) only 2
- (c) only 1
- (d) 2 and 3

© None.

$$Tuf = 0.281$$

4WR

$$= 0.681$$

mid poi  
FWR

$$= 0.812$$

FWR

bridge

$$HWR = 1.021$$

$$FWR <_{\text{mid}}^{\text{Bridge}} = 0.48$$

$\eta$

40

81.02


R.f

Q

In an ideal operational amplifier depicted in fig. the potential at node A is:

*tricks*

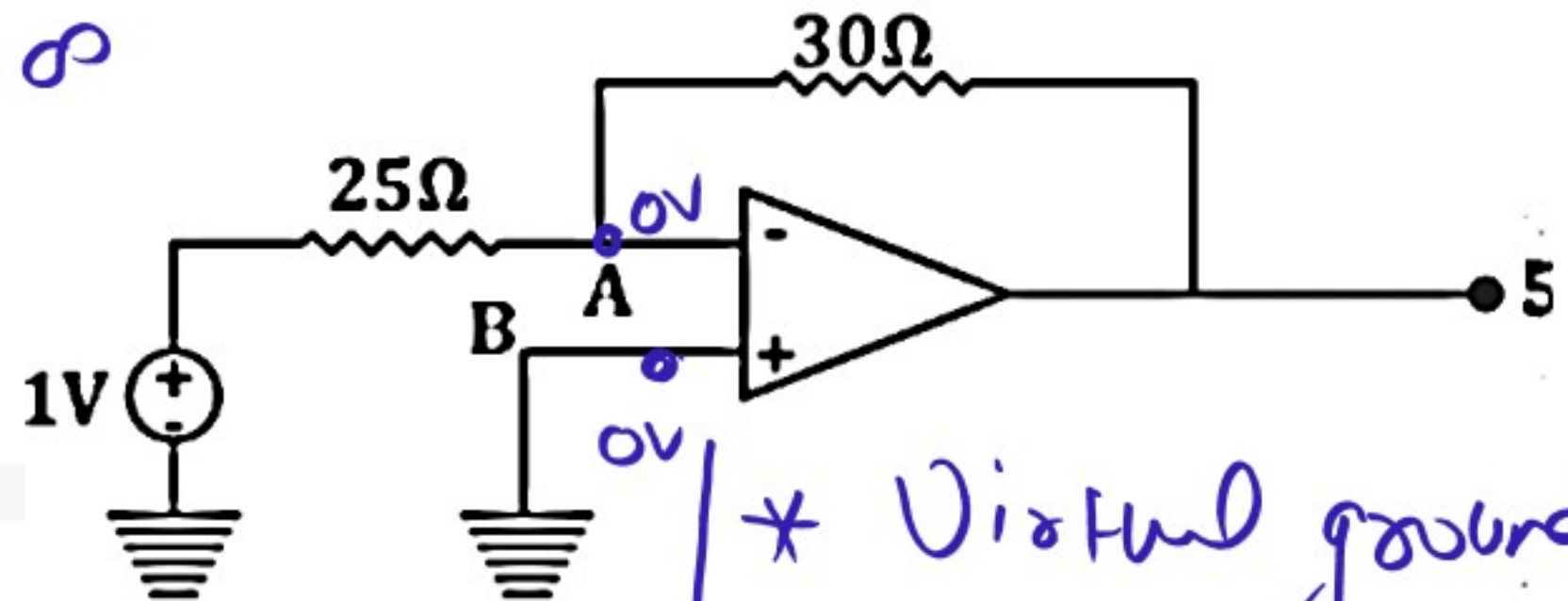*All things  $\infty = \infty$   
excluding  $R_o = 0$*



(a) 0 V

(b) 0.5 V

(c) 10 V

(d) can-not be determined.


*\* Virtual ground  
 $V_1 = V_2$*

*\*  $I_{in} = 0, R_{in} = \infty$*



Q

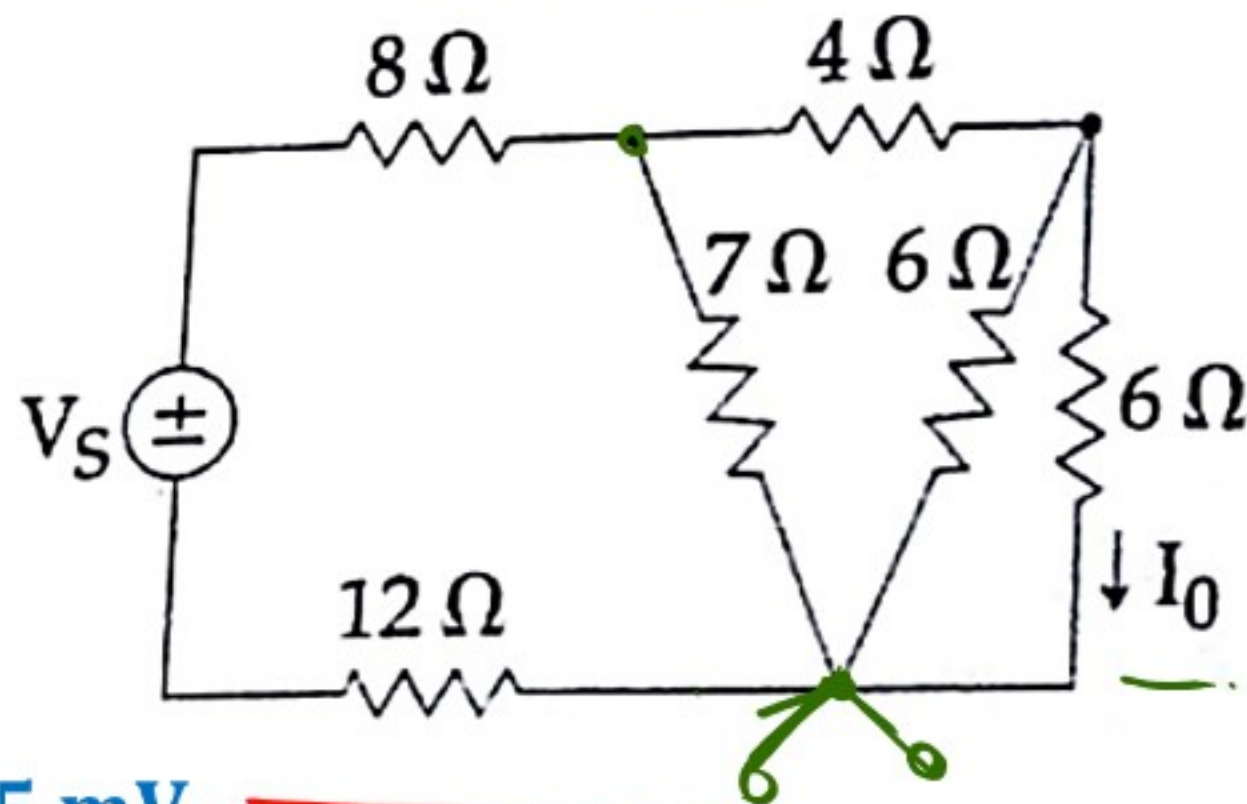For the network shown in the following figure the value of  $V_s$  which makes  $I_0 = 7.5$  mA is:



(a) 725 mV


(b) 680 mV

(c) 695 mV

 (d) 705 mV

$$V_2 = 60 + 45 = 105 \text{ V}$$

$$I_2 = \frac{105}{8}$$

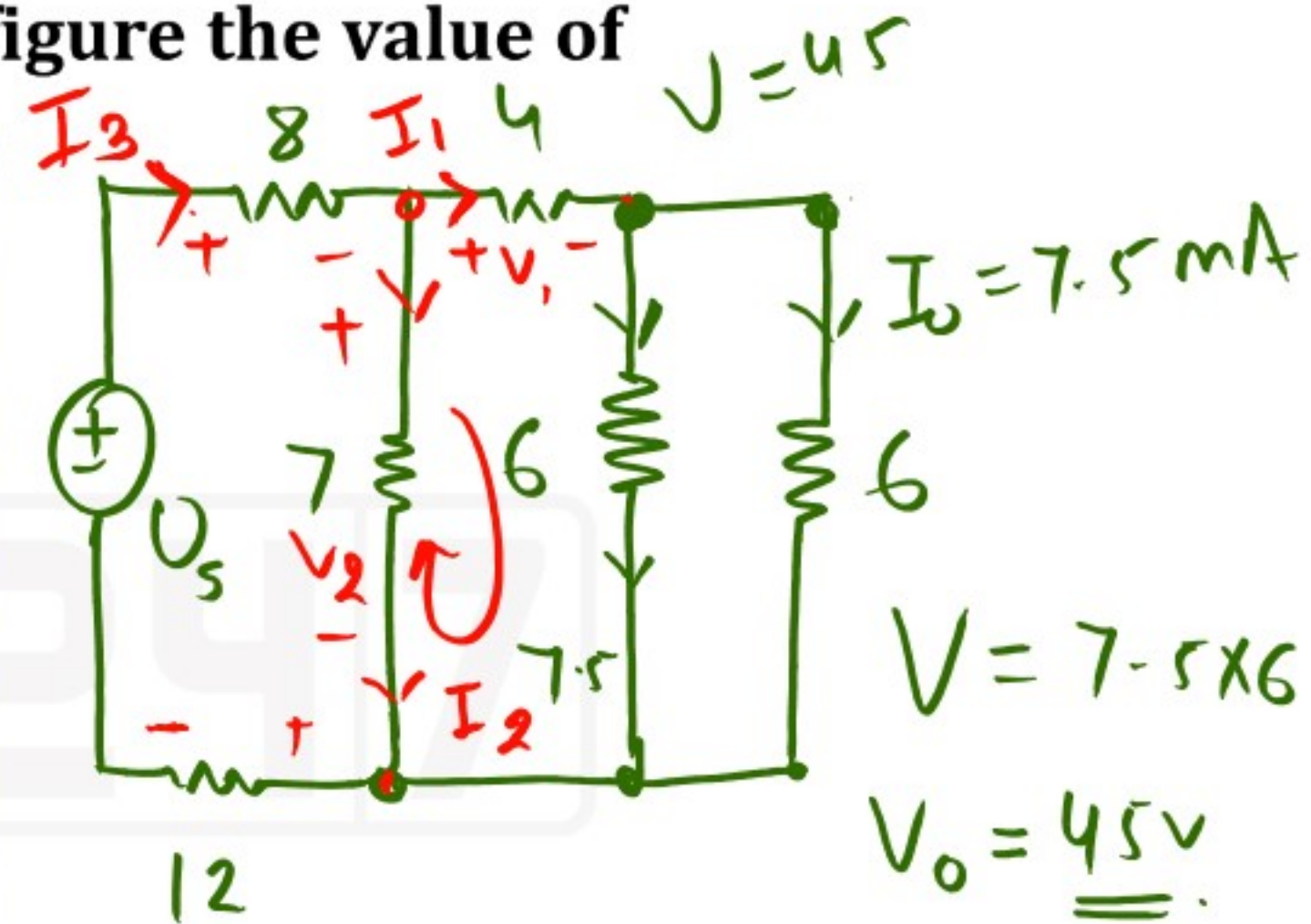

$$I_1 = 7.5 + 7.5 = 15 \text{ mA}$$

$$V_1 = 15 \times 4 = 60 \text{ mV}$$



Q

Tips easy

① - Round

② - Round

$$\frac{1}{\sqrt{2}}$$

$$\frac{1}{2\pi f}$$

In a fullwave rectifier, the load resistance  $R_L = 2 \text{ k}\Omega$ . Each diode has idealized characteristics having slope corresponding of  $400 \Omega$ . Voltage applied to each diode is  $240 \sin 50 t$ . V. Average value of load current will be

- (a) 82.00 mA  
 (b) 70.72 mA  
 (c) 63.84 mA  
 (d) 100.00 mA

2πf

$$\text{Slope} = V/I = 400 = R_d$$

$$V_o = \frac{2V_m}{\pi}$$

$$V_o = \frac{2 \times 240}{\pi}$$

$$V_o = 152.34 \dots$$

$$I_o = \frac{V_o}{2400}$$



Q

$A + A\bar{B} + A\bar{B}C + A\bar{B}C\bar{D}$  simplifies to:

(a)  $A + B$

(b)  $\bar{A} + B$

(c)  $A \cdot \bar{B}$

(d)  $A$

$$f = A + A\bar{B} + A\bar{B}C + A\bar{B}C\bar{D}$$

$$f = A [1 + \dots] = A$$


हमेशा 1

For a series Si diode configuration shown below the current  $I_D$  is:

Q

$$V_T = 0.7 \text{ Si}$$

$$= 0.3 \text{ Ge}$$

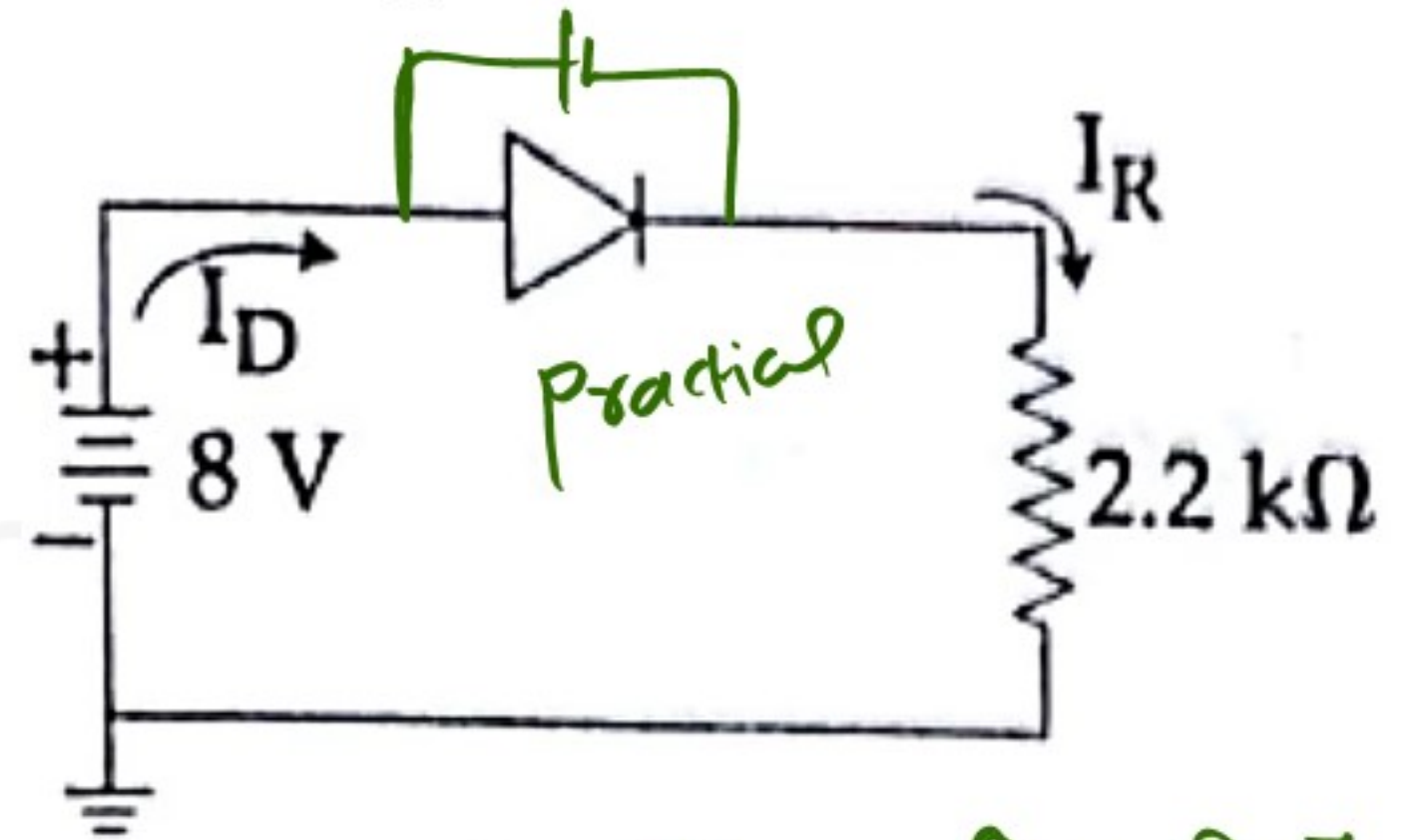

- (a) 3.32 mA
- (b) 3.95 mA
- (c) 3.63 mA
- (d) 3.64 mA


Ideal — ✓

$$I = \frac{8 - 0.7}{2.2}$$


$$I = 3.318$$



Q

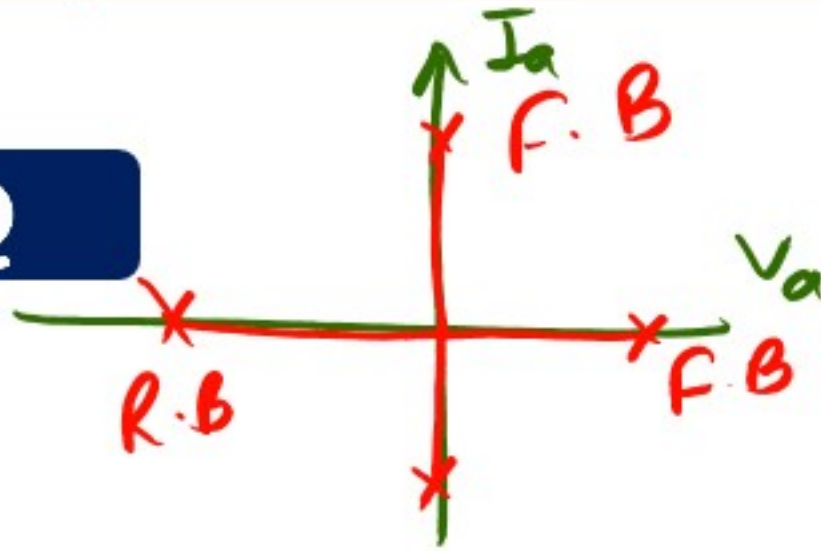


4-Quadrant

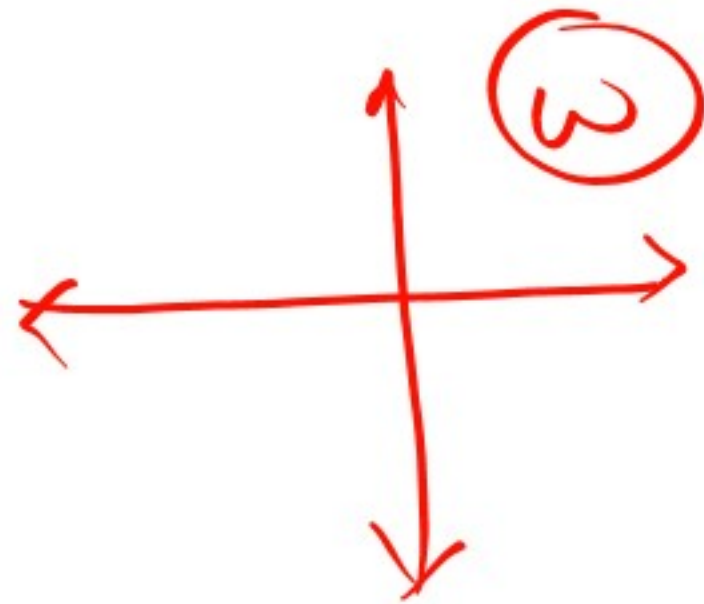

A TRIAC is:

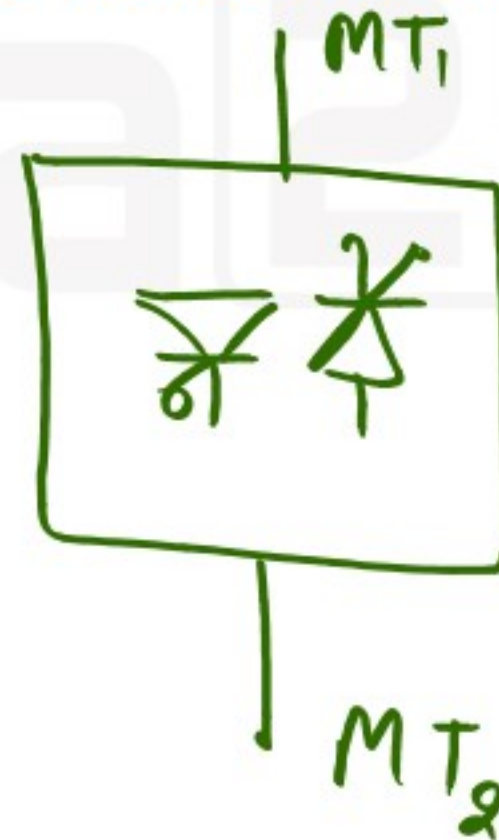- (a) bilateral device
- (b) two terminal device
- (c) unilateral device
- (d) four terminal device



two SCR  
\* Connected in Antiparallel

Q

The current gain of a Darlington pair in common emitter configuration is approximately:

(a)  $\frac{1+\beta}{1-\beta}$


(b)  $\frac{\beta}{1+\beta}$

(c)  $2\beta$

(d)  $\beta^2$





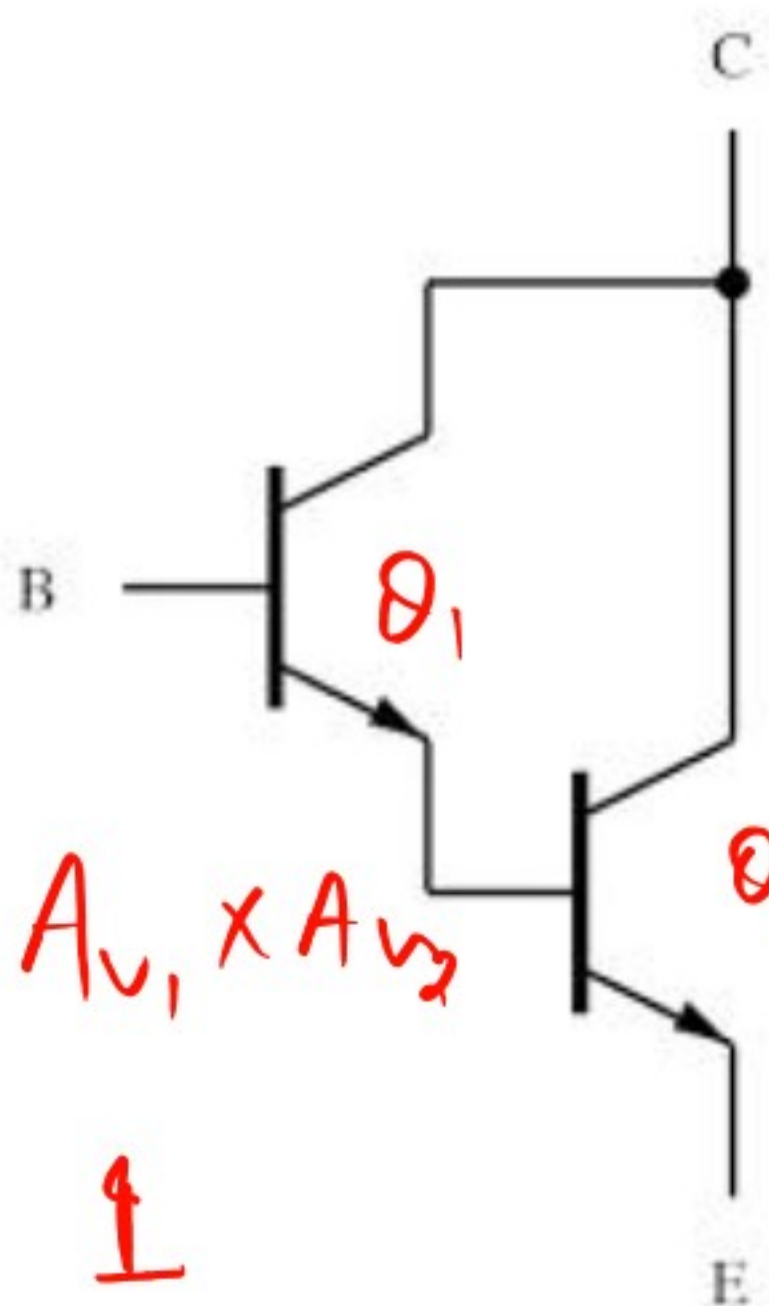

$$A_v = A_{v_1} \times A_{v_2}$$
$$= 1$$

$$A_i = h_{fe} \times h_{fe}$$
$$= h_{fe}^2 = \beta^2$$


In junction field effect transistor, the drain current can be approximated as:

$$(a) I_{DS} = \frac{I_{DSS}}{V_P} \left( 1 - \frac{V_{GS}}{2} \right)$$

$$(b) I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)$$

$$(c) I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^{\frac{1}{2}}$$
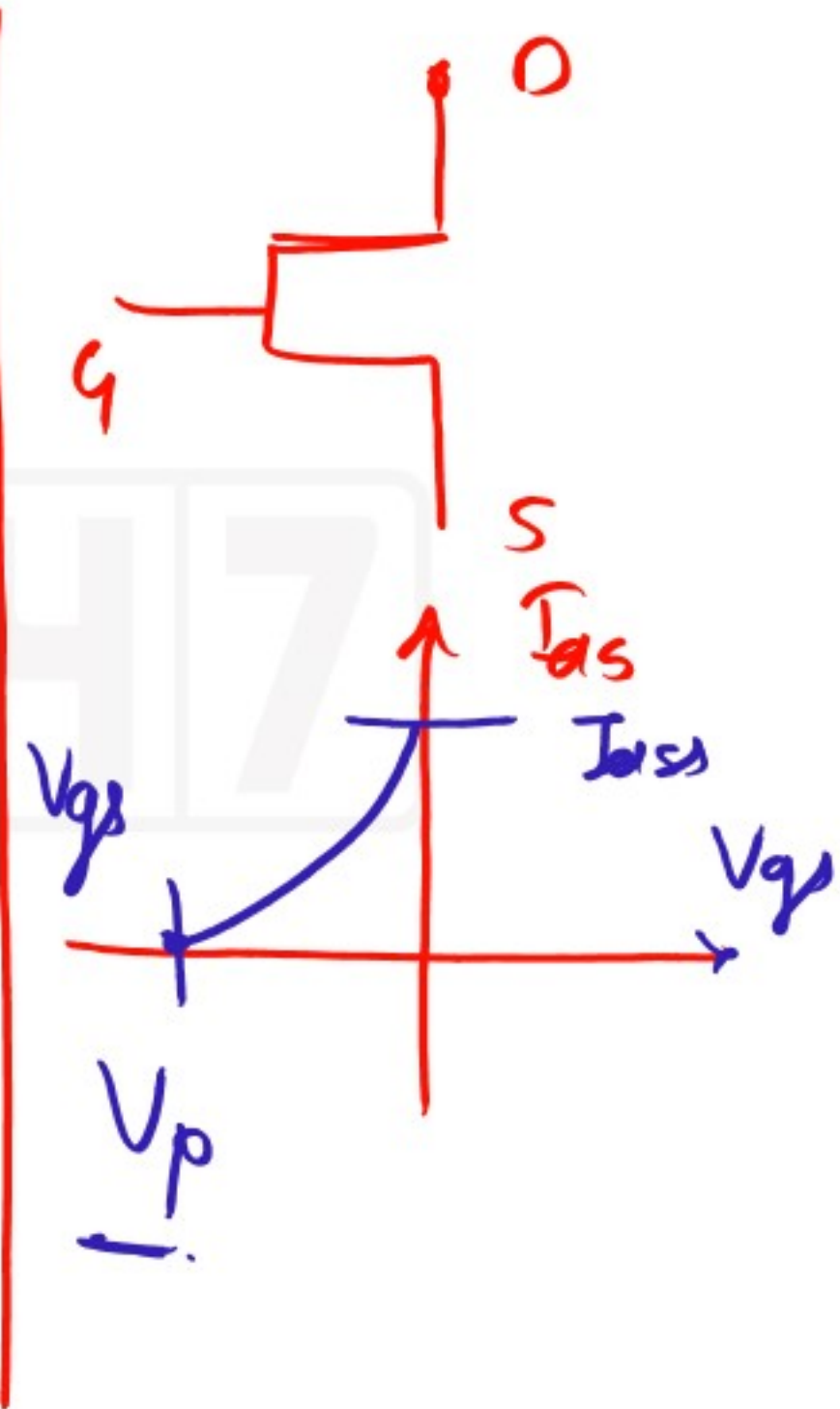
$$(d) I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$





Q

A PMMC meter has an internal resistance  $200 \Omega$  and the current required for its full scale deflection is  $50 \mu\text{A}$ . The meter is capable of measuring on its own a maximum voltage of:

- (a)  $10 \mu\text{V}$
- (b)  $5 \text{ mV}$
- (c)  $10 \text{ mV}$
- (d)  $5 \mu\text{V}$

$$\begin{aligned}V_m &= I_m R_m \\ &= 50 \times 10^{-6} \times 200 \\ &= 1000 \times 10^{-6} \\ &= 10 \text{ mV}\end{aligned}$$

Q

The voltage gain in a common emitter configuration is:

(a)  $-\frac{hfeR_L}{R_0}$


(b)  $-hfe$

(c)  $-\frac{hfeR_L}{R_i}$

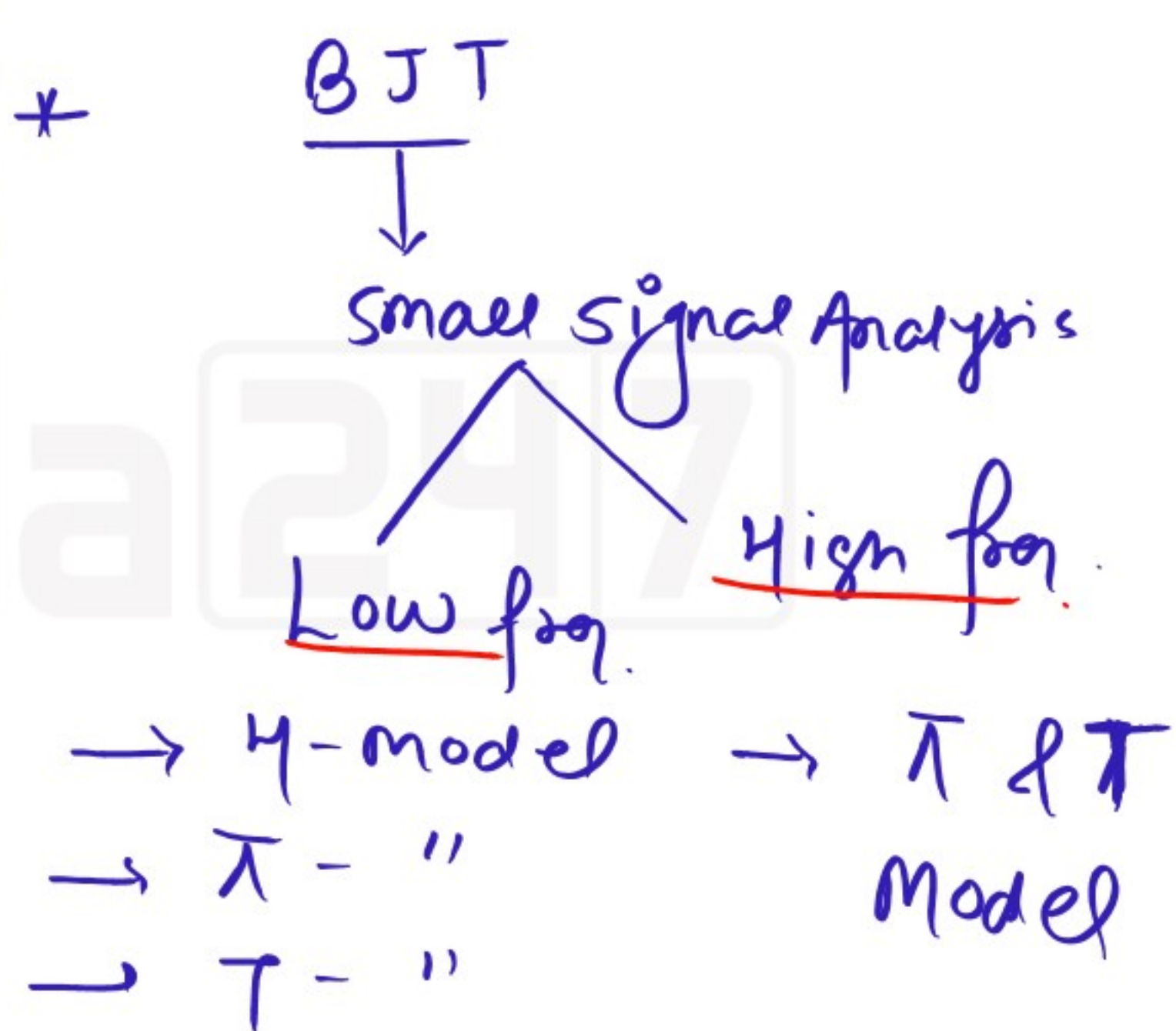(d)  $hie + (1 + hfe)R_e$

$hfe = \beta$

$$A_v = \frac{V_o}{V_i} = -\frac{hfe R_L}{R_i}$$





Q

In a voltage series feedback amplifier, if  $R_i$  is the input resistance without feedback. then input resistance with feedback is:

(a)  $R_{if} = \frac{R_i}{1+Av\beta}$


(b)  $R_{if} = R_i (1 - Av\beta)$

✓ (c)  $R_{if} = R_i (1 + Av\beta)$

(d)  $R_{if} = R_i$

\* f/b  $\rightarrow$  parallel  
 $\rightarrow$  Voltage  
 $\rightarrow$  Series  
 \* Current

feedback Amp.

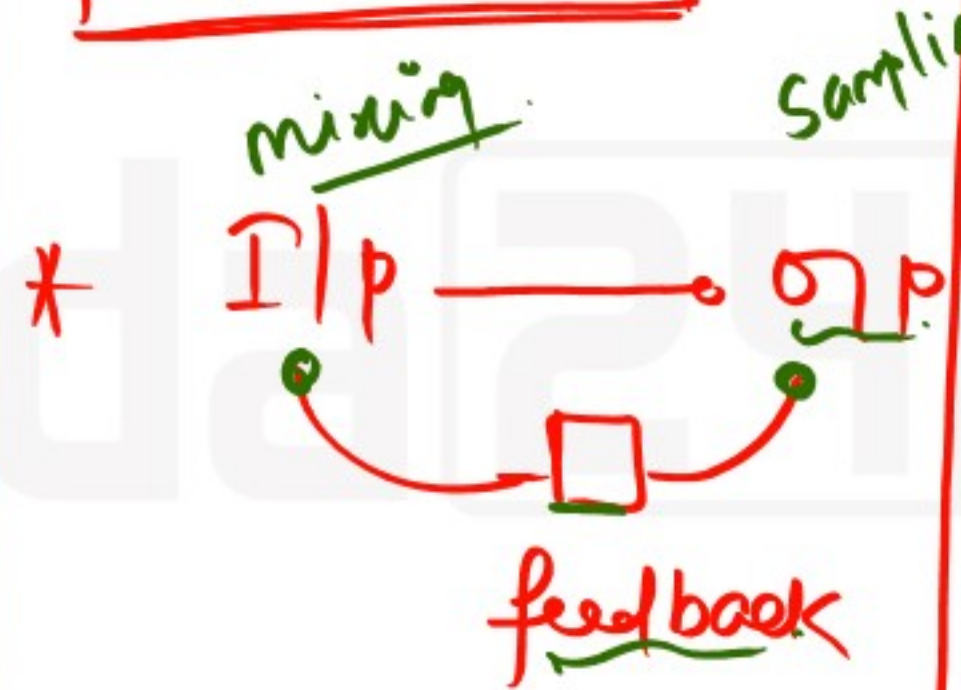

\*  $\text{Gain} \times \text{B.W.} = \text{const}$

B.W.  $\uparrow$ , Gain  $\downarrow$

$R_{if} = R_i (1 + A\beta)$

A = open gain

$\beta$  = feedback

\*  $R_{ref} = R_o / (1 + A\beta)$

Stab  $\uparrow$

Q

The induced emf in a coil is given as:

$$(a) e = L \frac{d\phi}{dt} \quad \phi$$

$$(b) e = L \frac{di}{dt}$$

$$(c) e = -L \frac{di}{dt}$$

$$(d) e = L \frac{d^2i}{dt^2}$$



$$V_L = L \frac{dI_L}{dt}$$

$$= \frac{\mu_0 \mu_r N^2 A}{l}$$

Lenz law



Q

An equivalent single current source between 'A' and 'B' in the following figure will be:


$I_N R_N$

(a) 1A, 5  $\Omega$

(b) 2A, 5  $\Omega$


(c) 1A, 10  $\Omega$

(d) 2A, 10  $\Omega$

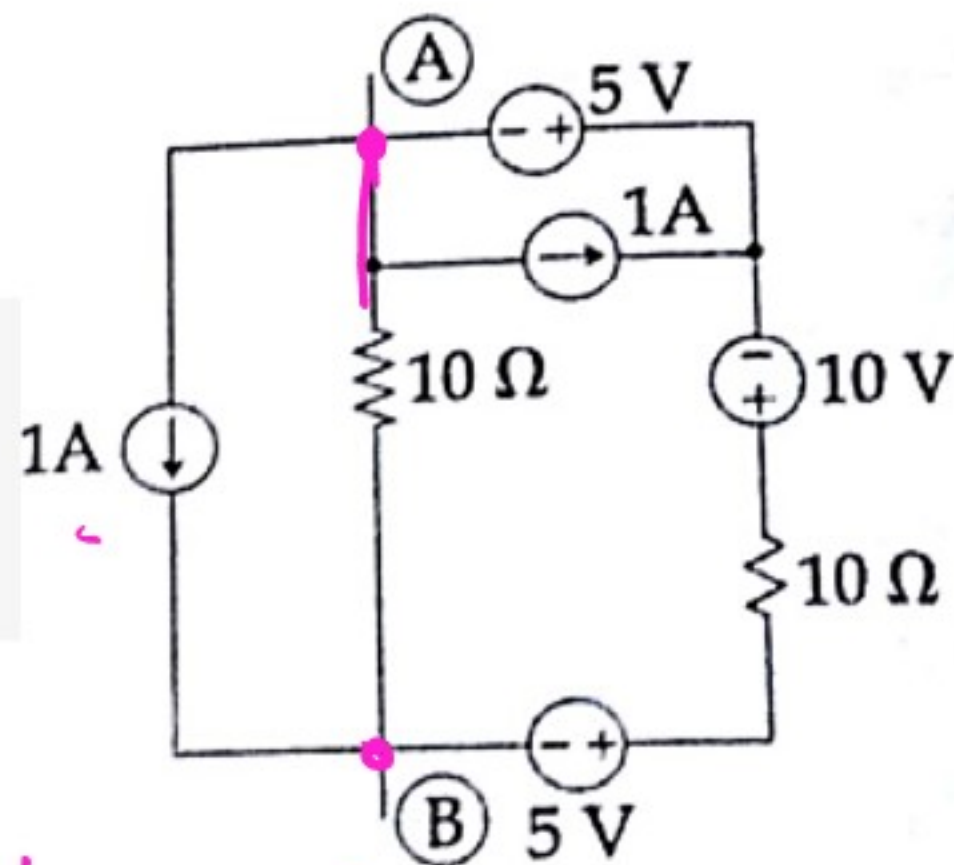

$$-5 - 10 + 10I + 5 = 0$$

$$I = 1$$

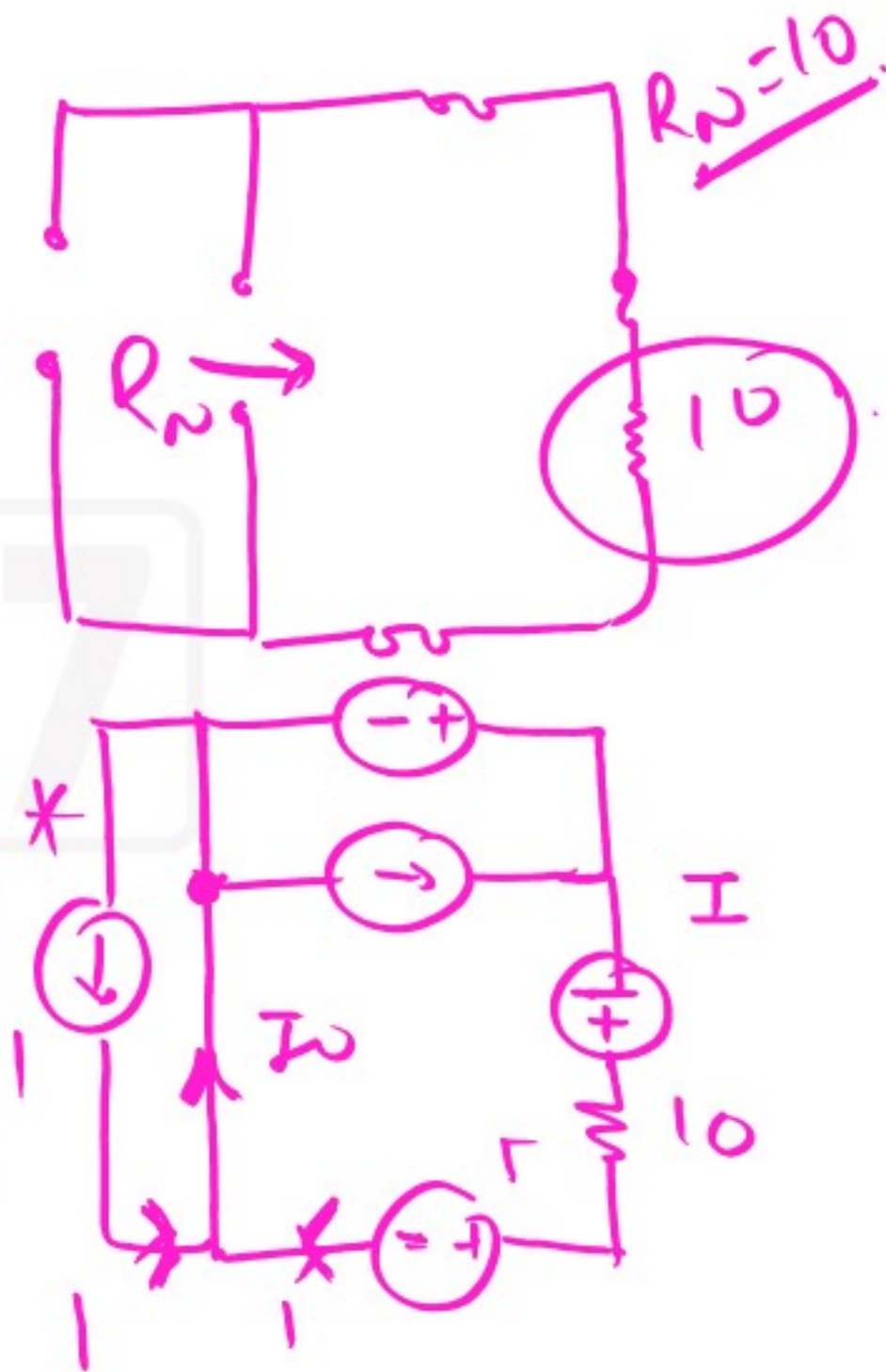

Q

The gain of an RC - Coupled amplifier decreases at high frequencies due to:

(a) Inter - electrode capacitance and shunt capacitance

(b) Coupling capacitors

(c) Emitter by pass capacitors

(d) Out capacitance of signal so

Gain ↓  $\rightarrow$   $f_{high}$   $\rightarrow$   $C_{inter}$   
 $C_p$   
Gain ↓  $f_{low}$   $\rightarrow$  Coupling  
 $C_p$



**Q** Consider the following statements regarding the formation of P-N junctions:

1. Holes diffuse across the junction from P side to N-side.
2. The depletion layer is wiped out.
3. There is a continuous flow of current.
4. A barrier potential is set up across the junction.


Which of the above statement are correct?

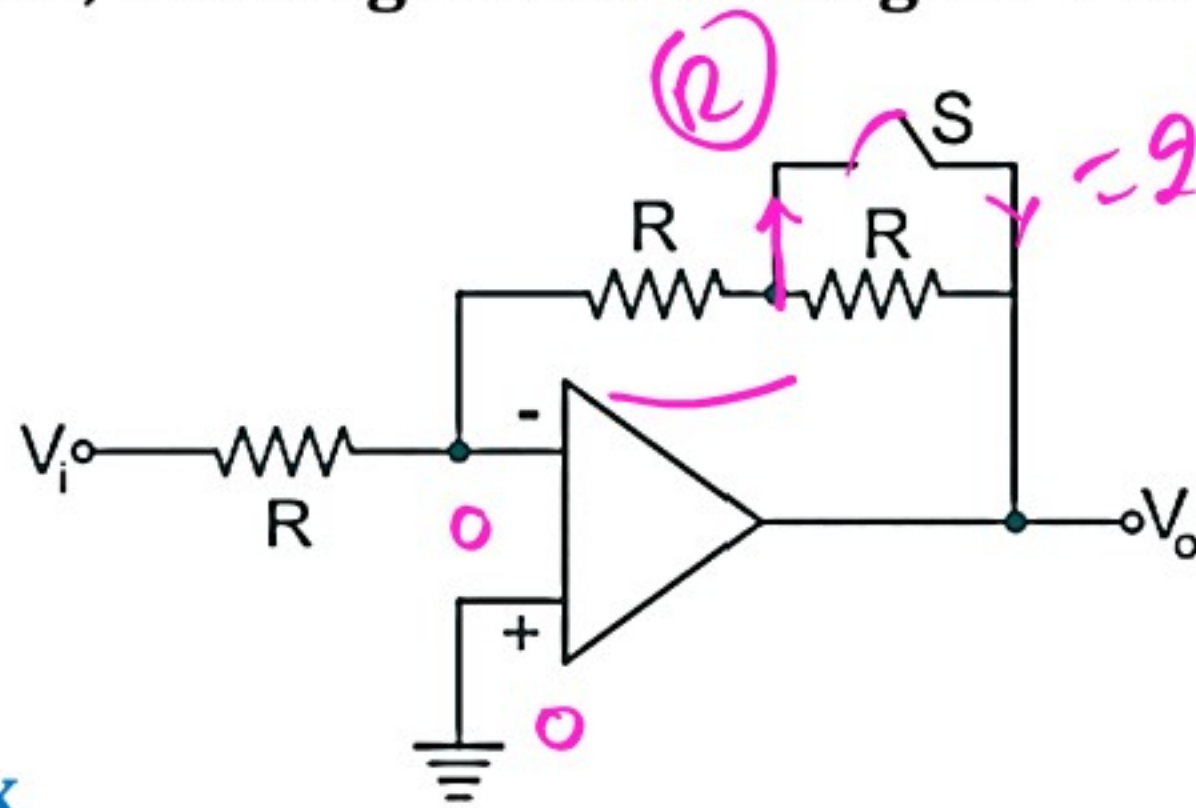- (a) 1 and 3  
(b) 2 and 3  
(c) 1 and 4  
(d) 2 and 4



Q

The magnitude of the gain  $\frac{v_0}{v_i}$  in the inverting op-amp circuit shown in the figure is  $x$  with switch  $S$  open. When switch  $S$  is closed, the magnitude of the gain will be



$$A_v = -\frac{R_2}{R_1}$$


$$x/2$$

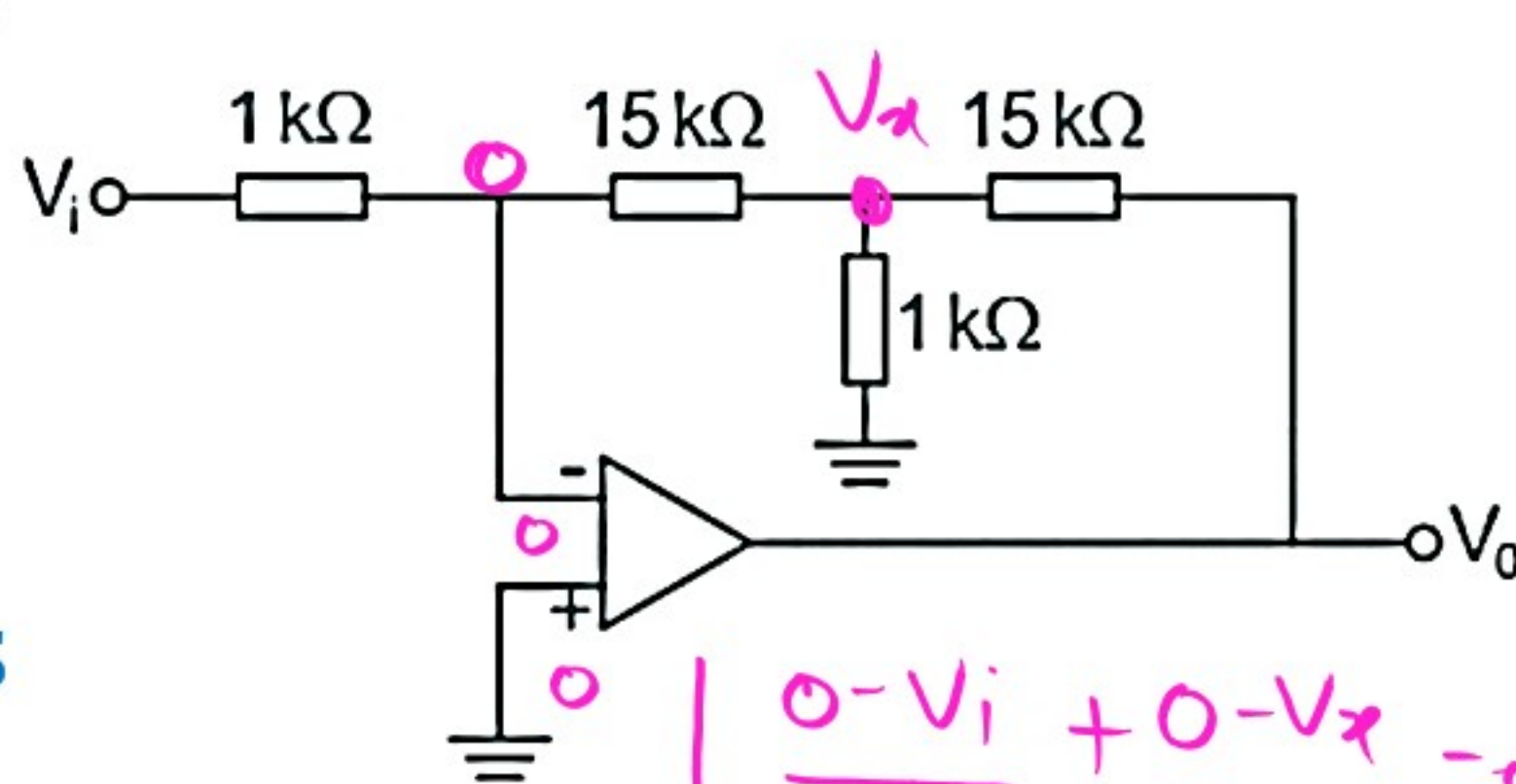(a)  $x$  (b)  $x/2$ (c)  $2x$ (d)  $2/x$



Q

What is the gain of the amplifier circuit as shown in the figure?



- (a) 255
- (b) 31
- (c) -3
- (d) -255

$$\frac{0 - V_i}{1} + \frac{0 - V_x}{15} = 0$$

$$V_i = -\frac{V_x}{15}$$

$$V_x = -15V_i$$

at  $V_x$ 

$$\frac{V_x - 0}{15} + \frac{V_x}{1} + \frac{V_x - V_o}{15} = 0$$

$$\frac{V_o}{V_i} = -255$$

Q

The Kirchhoff's current law works on the principle of conservation of

1. charge ✓

2. energy

3. power

Which of the above is/are correct?

✓ (a) 1 only

(b) 2 only

(c) 3 only

(d) 1, 2 and 3

$$\sum I_{in} = \sum I_{out}$$


$$I = \frac{Q}{t}$$



Q

A waveform shown in the figure is applied to a resistor of  $20 \Omega$ . The power dissipated in the resistor is

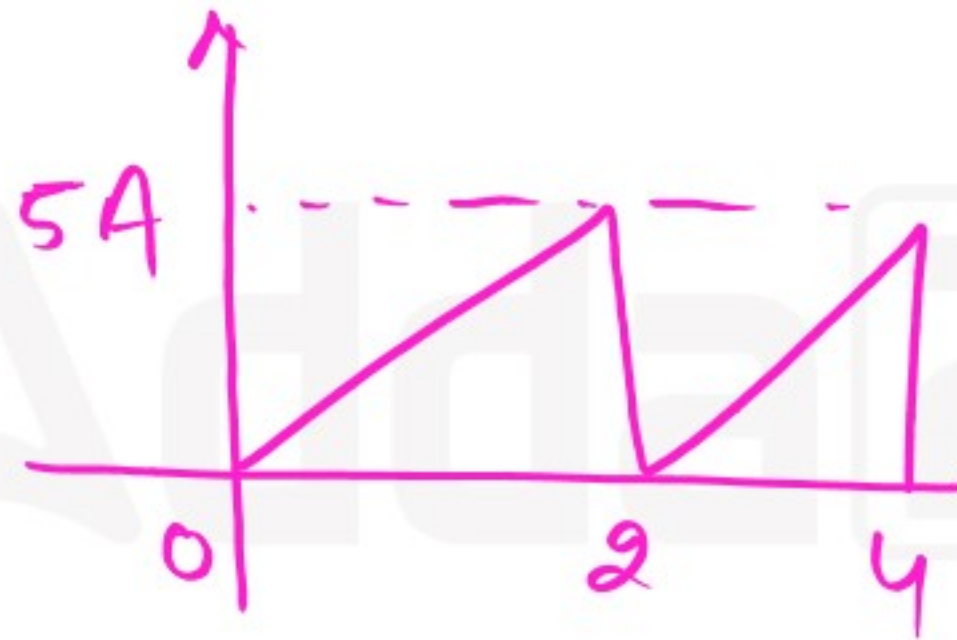- (a) 100 W
- (b) 600 W
- (c) 900 W
- (d) none



$$P_L = I_r^2 \cdot R$$

$$I_{\text{rms}} = \frac{I_m}{\sqrt{3}} = \frac{5}{\sqrt{3}}$$

$$P_L = \left( \frac{5}{\sqrt{3}} \right)^2 \times 20$$

Q

For what minimum value of propagation delay in each flip-flop will a 10-bit ripple counter skip a count, when it is clocked at 10 MHz?

- (a) 5 ns
- (b) 10 ns
- (c) 20 ns
- (d) 40 ns

$$f_{\min} = \frac{1}{n t_{pd}}$$

$n = \text{No. of Bit}$

$$t_{pd} = \frac{1}{f_{\max}} = \frac{1}{10 \times 10^6 \times 10}$$



Q

In a master-slave JK flip - flop

- (a) both master and slave are positive - edge-triggered
- (b) both master and slave are negative - edge-triggered
- (c) master is positive - edge - triggered and slave is negative - edge - triggered
- (d) master is negative - edge - triggered and slave is positive - edge - triggered

\* Race Around

Cond.  $J=1$   
 $K=1$

\* M-S - flip.  
⊕ ⊂ ⊃ ⊖

Q

When a transmission line section is first short - circuited, and then open - circuited, it shows input impedances of  $25 \Omega$  and  $100 \Omega$ , respectively. The characteristic impedance of the transmission line is

- (a)  $25 \Omega$
- (b)  $50 \Omega$
- (c)  $75 \Omega$
- (d)  $100 \Omega$

$$Z_c = \sqrt{Z_{sc} \times Z_{oc}}$$
$$= \sqrt{25 \times 100}$$



BILINGUAL

# The Foundation SSC JE 2023

**Electrical**

नीव आपके सिलेक्शन का



start Feb 6 2023 9 AM to 6 PM

BILINGUAL

## ELECTRICAL & ELECTRONICS ENGINEERING

### ka Mahapack

Live Class, Video Course  
Test Series, Ebooks

All in one

SSC-JET  
RRB-JE

4433

6 pm

4433

Yest

Tue